

**Unit I: Assessment: Assignments****Assignment – Lecture 26**

1. Power dissipated in a series RC circuit is 25 W, while the current and voltage being 0.4A and 230 V respectively. Find the value of capacitance.(Assume supply frequency of 50 Hz)