

## Unit I: Assessment Question Bank

### Lecture -30

1. Draw the phasor diagram for a parallel RLC circuit when

- i)  $B_L > B_C$
- ii)  $B_C > B_L$
- iii)  $B_L = B_C$