

UE25EE141A – UNIT 1 – ASSIGNMENT – ANSWER KEY

Lecture 1

1. i) $I_1 = 2A$, $I_2 = 1A$, $I_3 = 2A$
- ii) $X = 15\Omega$
- iii) $R_{eq} = 3\Omega$

Lecture 2

1. current through $500\Omega = 1.25mA$

Lecture 4

1. $R_{AB} = 4\Omega$

Lecture 5

- 1.

$$I_{AF} = 39A ; I_{FE} = -21A ; I_{ED} = 39A ; I_{DC} = -81A ; I_{CB} = -11A ; I_{BA} = -41A$$

Lecture 6

1. i) Load current = $0.967A$
- ii) Battery A absorbs $1.34A$
Battery B delivers $2.33A$
- iii) P.D across the Load = $9.67V$

Lecture 8

1. Current delivered by the source = $0.623A$

Lecture 9

1. $R_{AB} = 3.78\Omega$

Lecture 10

2. Considering both mesh currents clockwise, mesh currents are

$I_1 = 4A$ & $I_2 = 3.5A$

Hence, current through 4Ω resistor = $0.5A$

Lecture 11

2. Current through 5Ω resistor = $1A$

Lecture 12

1. Current due to $2V$ battery acting alone in 8Ω is $0.143A$

Current due to $2A$ source acting alone in 8Ω is $0.857A$

Hence, by SPT, Total current $I = I' + I'' = 1A$

Lecture 13

1. Current due to $5A$ source acting alone in 4Ω is $3.43A$

Current due to $20V$ battery acting alone in 4Ω is $0.857A$

Hence, by SPT, Total current $I = I' + I'' = 4.28A$

Lecture 14

1. $V_{TH} = 28.57V$; $R_{TH} = 8.57k\Omega$

Hence, Range of voltage across R_L varies between $15.3V$ to $20V$

Lecture 15

1. $V_{TH} = 12V$; $R_{TH} = 18\Omega$

Hence, Load current in branch BD will be $0.207A$ and flows from B to D

Lecture 16

1. $V_{TH} = 60V$; $R_{TH} = 9\Omega$

Hence, Range of current through R varies between 3.16A to 6A