

Unit I: Assessment: Assignments

Assignment – Lecture 31

1. A Resistor of 6Ω and an ideal inductor of 7.95mH are connected in parallel across 20V , 50 Hz supply. Determine
 - i) Branch currents and supply current in phasor form
 - ii) Draw phasor diagram