

Unit I: Assessment: Assignments**Assignment – Lecture 25**

1. Find the instantaneous expression for the current when a voltage represented by $v(t) = 283\sin 100\pi t$ Volts is applied to a coil having $R = 50\Omega$ and $L = 0.159H$.

Also find active, reactive and apparent powers in the network by using power triangle concept.