



# ELEMENTS OF ELECTRICAL ENGINEERING

Course Code : UE25EE141A/B

---

## FACULTY CONTRIBUTED:

Department of EEE, RR Campus

Prof . Jyothi T N  
Prof. Vadhiraj K P P  
Prof. Kruthika N  
Prof. Suma S  
Prof. Pushpa K R  
Prof. Sangeeta Modi

Department of ECE, EC Campus

Prof. Lokesh L  
Prof. Dhanashree G Bhate  
Dr. Renuka R Kajur  
Prof. Rajesh Chandrashekar  
Prof. Sangam Kumar G H

# **ELEMENTS OF ELECTRICAL ENGINEERING (UE25EE141A/B)**

---

## **Numerical Examples on Series AC Circuits**


Jyothi T N

Department of Electrical & Electronics Engineering

### Question:

A capacitor is used in series with a tungsten- filament bulb rated at 500W,100V, so that it gives its rated illumination when connected to a 220V,50Hz supply. Calculate the value of the capacitance, current drawn from the supply. Find the power factor.

Solution:

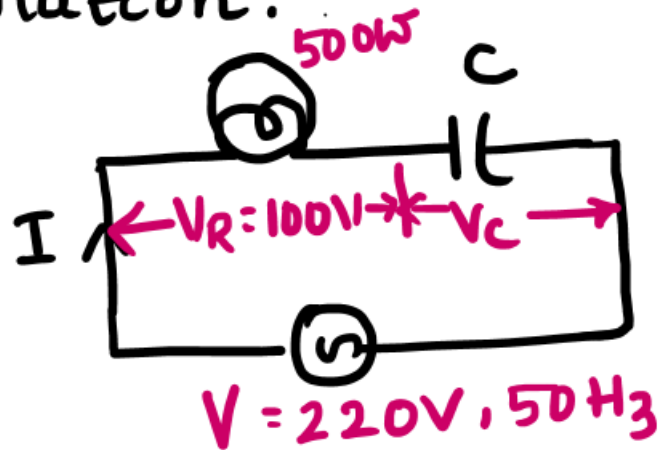

$$V^2 = V_R^2 + V_C^2$$

$$V_C^2 = 220^2 - 100^2$$

$$V_C = 195.95V$$


$$I_{\text{Bulb}} = \frac{P}{V} = \frac{500}{100} = 5A$$

Since it is a series network, current is same in all the elements. Hence current drawn is 5A.

$$X_C = \frac{V_C}{I} = \frac{195.95}{5} = 39.19\Omega$$

$$C = \frac{1}{2\pi f X_C} = 81.27\mu F$$

Solution:

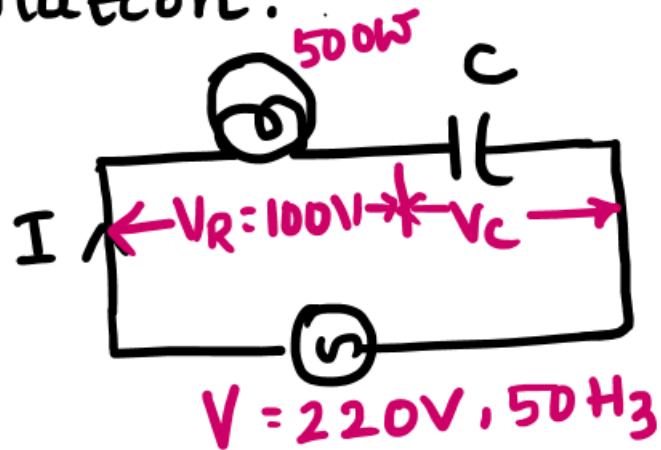

$$\text{Pf, } \cos \phi = \frac{P}{S}$$

$$\cos \phi = \frac{500}{220 \times 5} = 0.4545 \text{ lead}$$


Phasor dia



### Question:

**3 coils A,B and C are connected in series. When a current of 3A is passed through the circuit, the voltage drops are respectively 12V, 6V and 9V on direct current and 15V, 9V and 12V on alternating current. Find for each of the coils i) internal parameters, ii) power dissipated when alternating current flows through the circuit, (iii) the applied voltage across it. Draw the phasor diagram. Find the overall power factor of the circuit.**

Solution :

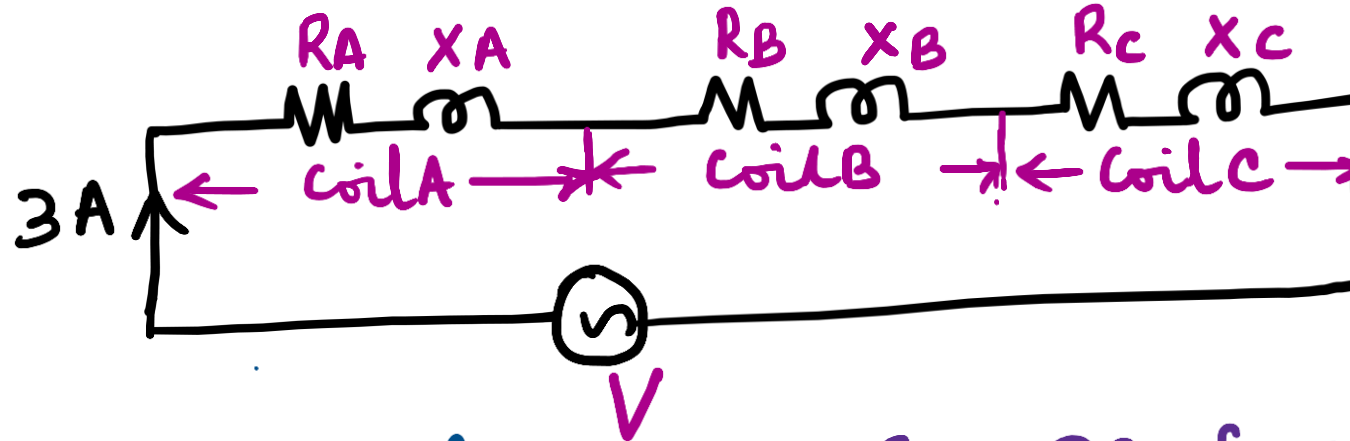

on DC

$$V_A = 12V$$

$$V_B = 6V$$

$$V_C = 9V$$

on AC

$$V_A = 15$$

$$V_B = 9V$$

$$V_C = 12V$$

For DC  $f=0$ ,  $X_L=0$   
 $\therefore$  coil behaves like a  
Pure resistor  $\therefore$

$$R_A = V_A / I = 12/3 = 4\Omega$$

$$R_B = V_B / I = 6/3 = 2\Omega$$

$$R_C = V_C / I = 9/3 = 3\Omega$$

For AC supply

$$Z_A = V_A / I = 15 / 3 = 5 \Omega \quad ; \quad X_A = \sqrt{Z_A^2 - R_A^2} = \sqrt{5^2 - 4^2} = 3 \Omega$$

$$Z_B = V_B / I = 9 / 3 = 3 \Omega \quad ; \quad X_B = \sqrt{Z_B^2 - R_B^2} = \sqrt{3^2 - 2^2} = 2.23 \Omega$$

$$Z_C = V_C / I = 12 / 3 = 4 \Omega \quad ; \quad X_C = \sqrt{Z_C^2 - R_C^2} = \sqrt{4^2 - 3^2} = 2.64 \Omega$$

$$\vec{I} = 3 \angle 0^\circ \text{ (Reference)}$$

$$\vec{V}_A = \vec{I} Z_A = 3(4 + j3) = 15 \angle 36.86^\circ$$

$$\vec{V}_B = \vec{I} Z_B = 3(2 + j2.23) = 8.98 \angle 48.11^\circ$$

$$\vec{V}_C = \vec{I} Z_C = 3(3 + j2.64) = 11.99 \angle 41.35^\circ$$



Applied voltage  $\vec{V} = \vec{V}_A + \vec{V}_B + \vec{V}_C$

$$= 15 \angle 36.86^\circ + 8.98 \angle 48.11^\circ + 11.99 \angle 41.35^\circ$$
$$= 35.86 \angle 41.16^\circ$$

Power dissipated  $= I^2 R_T$

$$= 3^2 (4+2+3)$$
$$= 81 \text{ W}$$

Overall Pf  $= \cos(41.16^\circ)$


$$= 0.752 \text{ lag}$$

# ELEMENTS OF ELECTRICAL ENGINEERING

## Numerical Example 2



Phasor diagram:

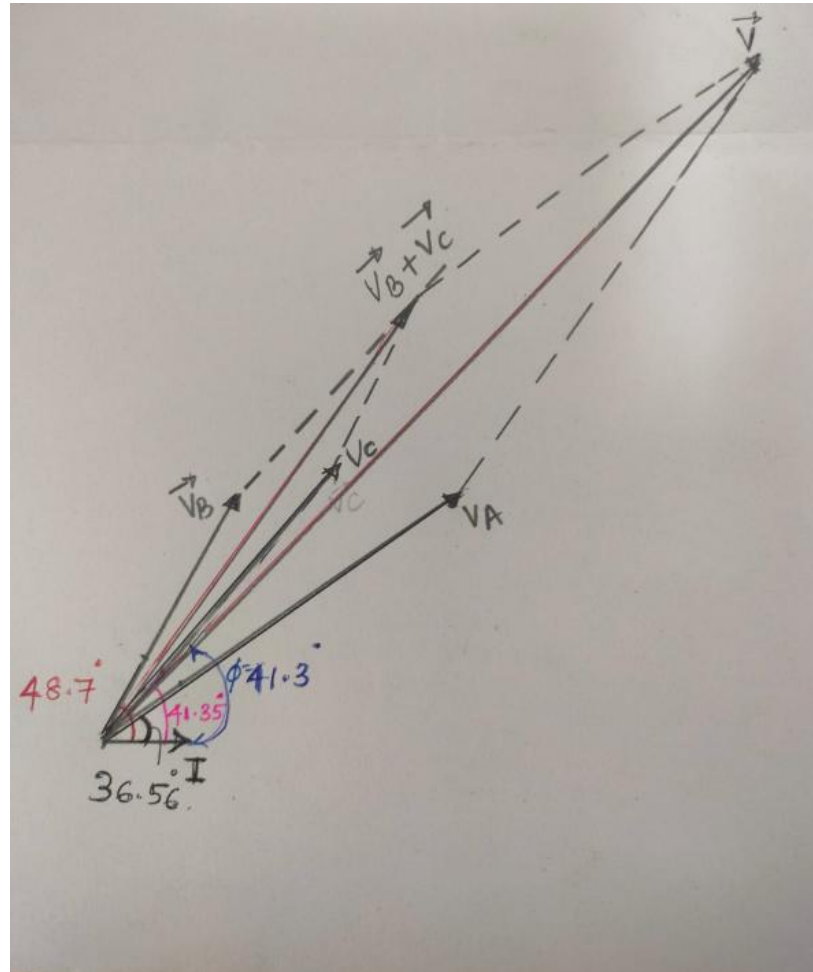

$$V_A \angle \phi_A = 15 \angle 36.56$$

$$V_B \angle \phi_B = 9 \angle 48.7$$

$$V_C \angle \phi_C = 12 \angle 41.7$$

$$I \angle 0 = 3 \angle 0 \text{ (Reference)}$$

$$V \angle \phi = 35.85 \angle 41.3$$

### Text Book:

1. “Basic Electrical Engineering” S.K Bhattacharya, 1<sup>st</sup>Edition Pearson India Education Services Pvt. Ltd., 2017
2. “Basic Electrical Engineering”, D. C. Kulshreshta, 2<sup>nd</sup>Edition, McGraw-Hill. 2019
3. “Special Electrical Machines” E G Janardanan, PHI Learning Pvt. Ltd., 2014

### Reference Books:

1. “Engineering Circuit Analysis” William Hayt, Jack Kemmerly, Jamie Phillips and Steven Durbin, 10th Edition McGraw Hill, 2023
2. “Electrical and Electronic Technology” E. Hughes (Revised by J. Hiley, K. Brown & I.M Smith), 12th Edition, Pearson Education, 2016.



# THANK YOU

---

**Jyothi T.N**

Department of Electrical & Electronics Engineering

**[jyothitn@pes.edu](mailto:jyothitn@pes.edu)**