

## NOTES Class-47

### Variation in Wattmeter readings with power factor of the load

#### Variation in wattmeter readings – Inductive load

For inductive loads,  $W_1 = V_L \cdot I_L \cdot \cos(30+\phi)$  &  $W_2 = V_L \cdot I_L \cdot \cos(30-\phi)$

As phase angle  $\phi$  increases, load power factor decreases.

With an increase in the phase angle  $\phi$ ,  $W_1 = V_L \cdot I_L \cdot \cos(30+\phi)$  decreases &

$W_2 = V_L \cdot I_L \cdot \cos(30-\phi)$  increases.

Phase Angle, $\phi$	Load Power factor, $\cos\phi$	$W_1 = V_L I_L \cos(30+\phi)$	$W_2 = V_L I_L \cos(30-\phi)$	Comments
$0^\circ$	1	$\frac{\sqrt{3}V_L I_L}{2}$	$\frac{\sqrt{3}V_L I_L}{2}$	$W_1 = W_2$
$30^\circ$	0.866 Lag	$\frac{V_L I_L}{2}$	$V_L I_L$	$W_1 = \frac{W_2}{2}$
$60^\circ$	0.5 Lag	0	$\frac{\sqrt{3}V_L I_L}{2}$	$W_1 = 0;$ $W_2 = P_{3\text{-phase}}$
$>60^\circ$	$< 0.5$ Lag	Negative	Positive	$W_1 = \text{-ve};$ $W_2 = \text{+ve}$

#### Important observations:


- When phase angle is  $<60^\circ$  (or) power factor of the load is  $> 0.5$  Lag, both the wattmeters read positive readings.
- When phase angle =  $60^\circ$  (or) power factor of the load is = 0.5 Lag, one of the wattmeters reads zero and the other reads the total three phase active power.

- When phase angle is  $>60^\circ$  (or) power factor of the load is  $< 0.5$  Lag, one of the wattmeters reads negative i.e., its pointer moves behind zero. To

record its reading, either reverse its CC connections or PC connections (not both) & record this value with a negative sign.

## Variation in wattmeter readings – Capacitive load

Now, consider capacitive Loads

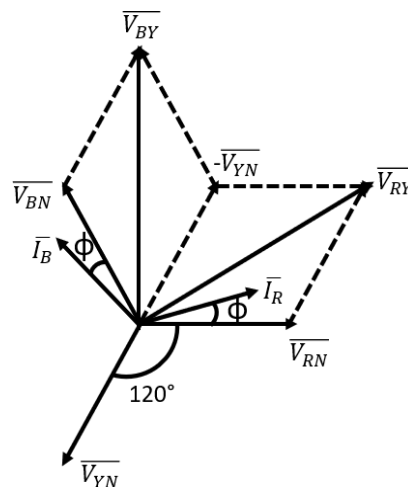

For this case,  $W_1 = V_{RY} \cdot I_R \cdot \cos(30^\circ - \phi)$  &  $W_2 = V_{BY} \cdot I_B \cdot \cos(30^\circ + \phi)$

Phase Angle, $\phi$	Load Power factor, $\cos\phi$	$W_1 = V_L I_L \cos(30^\circ - \phi)$	$W_2 = V_L I_L \cos(30^\circ + \phi)$	Comments
$0^\circ$	1	$\frac{\sqrt{3} V_L I_L}{2}$	$\frac{\sqrt{3} V_L I_L}{2}$	$W_1 = W_2$
$30^\circ$	0.866 Lead	$V_L I_L$	$\frac{V_L I_L}{2}$	$W_2 = \frac{W_1}{2}$
$60^\circ$	0.5 Lead	$\frac{\sqrt{3} V_L I_L}{2}$	0	$W_1 = P_{3\text{-phase}};$ $W_2 = 0$
$>60^\circ$	$< 0.5$ Lead	Positive	Negative	$W_1 = +ve;$ $W_2 = -ve$

Thus, the readings become just the opposite to that of inductive load case.

### **Numerical Example 1**

#### **Question:**

In a two wattmeter method of measuring three phase power, it is observed that the wattmeter readings are in the ratio of 3:1. Determine the power factor of the Load.

#### **Solution:**

##### **Given Data:**

$$W_1 : W_2 = 3:1$$

$$\text{Power factor} = \cos\phi = \cos\left(\tan^{-1}\left(\frac{\sqrt{3}(W_1 - W_2)}{W_1 + W_2}\right)\right)$$

Therefore, Power factor = 0.756

### **Numerical Example 2**

#### **Question:**

Two wattmeters are connected to measure input to a balanced three phase circuit indicate 2000W and 500W respectively. Find the power factor when

- i) Both readings are positive
- ii) Latter reading is obtained after reversing its CC

#### **Solution:**

**Case 1:**  $W_1 = 2000\text{W}$ ;  $W_2 = 500\text{W}$

$$\text{Power factor} = \cos\left(\tan^{-1}\left(\frac{\sqrt{3}(W_1 - W_2)}{W_1 + W_2}\right)\right) = 0.693$$

**Case 2:**  $W_1 = 2000\text{W}$ ;  $W_2 = -500\text{W}$

$$\text{Power factor} = \cos\left(\tan^{-1}\left(\frac{\sqrt{3}(W_1 - W_2)}{W_1 + W_2}\right)\right) = 0.327$$