

Unit III: Assessment: Q & A (Selected)

Lecture 44

1. A balanced 3 ϕ star connected load is supplied from a symmetrical 3 ϕ 400V system. The current in each phase is 30A and lags by 30° behind the voltage. Find
i) Impedance in each phase ii) total power drawn. Draw phasor diagram.

Solution:

Given $V_L = 400V$, $V_{ph} = 230.9V$

$$I_{ph} = 30A$$

$$\phi = 30^\circ , \cos \phi = 0.866 \text{ lag}$$

$$\begin{aligned} \text{Impedance } Z_{ph} &= \frac{V_{ph}}{I_{ph}} \\ &= \frac{230.9}{30} \\ Z_{ph} &= 7.698 \Omega \end{aligned}$$

$$\begin{aligned} \text{Power} &= \sqrt{3} V_L I_L \cos \phi \\ &= \sqrt{3} (400) (30) 0.866 \\ &= 18 \text{ KW} \end{aligned}$$