

ELEMENTS OF ELECTRICAL ENGINEERING

Course Code : UE25EE141A/B



FACULTY CONTRIBUTED:

Department of EEE, RR Campus

Prof . Jyothi T N
Prof. Vadhiraj K P P
Prof. Kruthika N
Prof. Suma S
Prof. Pushpa K R
Prof. Sangeeta Modi

Department of ECE, EC Campus

Prof. Lokesh L
Prof. Dhanashree G Bhate
Dr. Renuka R Kajur
Prof. Rajesh Chandrashekar
Prof. Sangam Kumar G H

ELEMENTS OF ELECTRICAL ENGINEERING (UE25EE141A/B)




Analysis of series RC circuit with Impedance and power triangles

Jyothi T N

Department of Electrical & Electronics Engineering

Series RC Circuit

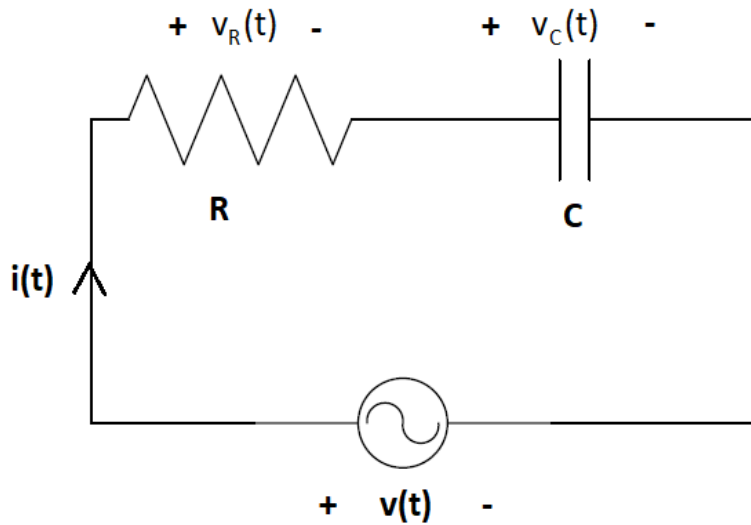

By KVL, $v(t) = v_R(t) + v_C(t)$

In Phasor form, $\bar{V} = \bar{V}_R + \bar{V}_C$

$$\bar{V}_R = \bar{I} * R$$


$$\bar{V}_C = \bar{I} * (-jX_C)$$

$$\bar{V} = \bar{I} * (R - jX_C)$$

Series RC Circuit

$$Z_T = \frac{\bar{V}}{\bar{I}} = (R - jX_C) = \sqrt{R^2 + X_C^2} \angle -\tan^{-1}\left(\frac{X_C}{R}\right)$$

Phasor Diagram:

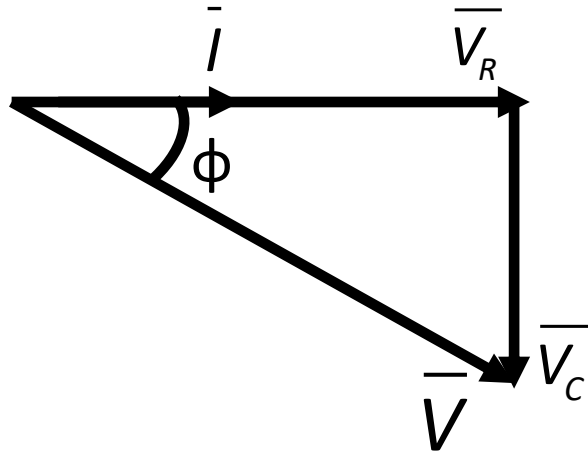

Phase angle of a network is found as

$$\phi = \angle \bar{V} - \angle \bar{I}$$

$$\phi = -\tan^{-1}\left(\frac{|\bar{V}_C|}{|\bar{V}_R|}\right) = -\tan^{-1}\left(\frac{V_C}{V_R}\right) = -\tan^{-1}\left(\frac{X_C}{R}\right)$$


Negative phase angle means voltage lags current.

In series AC networks, phase angle = Impedance angle.


ELEMENTS OF ELECTRICAL ENGINEERING

Impedance & Power Triangles – Series RC Circuit

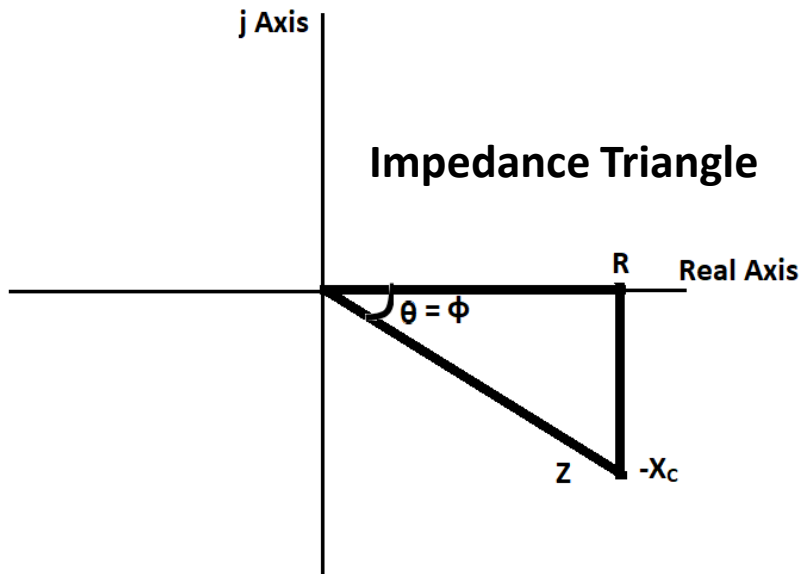For a series RC circuit, $Z = R - jX_C = \sqrt{R^2 + X_C^2} \angle -\tan^{-1}\left(\frac{X_C}{R}\right)$



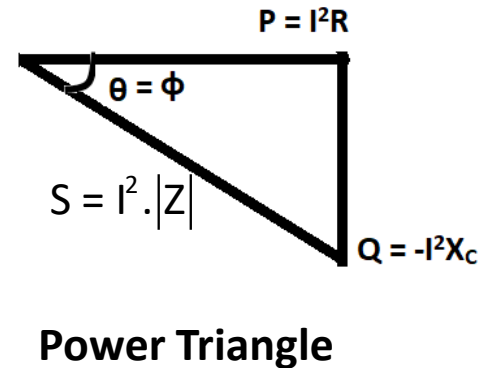Impedance Triangle of a series RC circuit lies Quadrant IV of complex plane.



$$P = VI \cos \phi = (I \cdot |Z|) \cdot I \cdot \frac{R}{|Z|} = I^2 R$$

$$Q = VI \sin \phi = (I \cdot |Z|) \cdot I \cdot \frac{-X_C}{|Z|} = -I^2 X_C$$

$$S = VI = (I \cdot |Z|) \cdot I = I^2 |Z|$$

Question:

A series RC circuit with $R = 4\Omega$, $C = 120\mu\text{F}$ is connected across 230V, 50 Hz supply. Calculate the current drawn by the circuit. Draw the phasor diagram.

Step 1: Calculate Capacitive Reactance (X_C)

$$X_C = \frac{1}{2\pi fC}$$

$$X_C = \frac{1}{2\pi \times 50 \times 120 \times 10^{-6}}$$

$$X_C = \frac{1}{2\pi \times 0.006}$$

$$X_C = \frac{1}{0.0377}$$

$$X_C \approx 26.5 \Omega$$

Step 2: Calculate Total Impedance (Z)

$$Z = \sqrt{R^2 + X_C^2}$$

$$Z = \sqrt{4^2 + 26.5^2} = \sqrt{16 + 702.25} = \sqrt{718.25}$$

$$Z \approx 26.8 \Omega$$

Step 3: Calculate Circuit Current (I)

$$I = \frac{V}{Z} = \frac{230}{26.8} \approx 8.58 \text{ A}$$

Text Book:

1. “Basic Electrical Engineering” S.K Bhattacharya, 1stEdition Pearson India Education Services Pvt. Ltd., 2017
2. “Basic Electrical Engineering”, D. C. Kulshreshta, 2ndEdition, McGraw-Hill. 2019
3. “Special Electrical Machines” E G Janardanan, PHI Learning Pvt. Ltd., 2014

Reference Books:

1. “Engineering Circuit Analysis” William Hayt, Jack Kemmerly, Jamie Phillips and Steven Durbin, 10th Edition McGraw Hill, 2023
2. “Electrical and Electronic Technology” E. Hughes (Revised by J. Hiley, K. Brown & I.M Smith), 12th Edition, Pearson Education, 2016.



THANK YOU

Jyothi T.N

Department of Electrical & Electronics Engineering

jyothitn@pes.edu