

Lecture 41

2. It is observed that first phase voltage in a balanced star system is $100\sin(\omega t + 10^\circ)\text{V}$. Express all the three phase voltages and all the three line voltages in both time form and phasor form

Solution:

Given: $V_{RN}(t) = 100\sin(\omega t + 10^\circ)\text{V}$

In a balanced 3 ϕ system, second phase voltage lags first phase voltage by 120° & Third phase voltage lags first phase voltage by 240° .

$$\therefore V_{YN}(t) = 100\sin(\omega t + 10^\circ - 120^\circ) \\ = 100\sin(\omega t - 110^\circ)\text{V}$$

$$V_{BN}(t) = 100\sin(\omega t + 10^\circ - 240^\circ) \\ = 100\sin(\omega t - 230^\circ)\text{V}$$

Each line voltage is $\sqrt{3}$ Vph and leads corresponding phase voltage by 30° .

Since $V_{RN}(t) = 100\sin(\omega t + 10^\circ)$

$$\Rightarrow V_{RY}(t) = \sqrt{3} \times 100\sin(\omega t + 10^\circ + 30^\circ) \\ = 173.20\sin(\omega t + 40^\circ)\text{V}$$

Unit III: Assessment: Q & A (Selected)

Similarly 2nd line voltage lags 1st line voltage by 120° & 3rd line voltage lags 1st line voltage by 240° .

Hence
$$V_{YB}(t) = \sqrt{3} \times 100 \sin(\omega t + 40^\circ - 120^\circ)$$
$$= 173.20 \sin(\omega t - 80^\circ) \text{ V}$$

$$V_{BR}(t) = \sqrt{3} \times 100 \sin(\omega t + 40^\circ - 240^\circ)$$
$$= 173.20 \sin(\omega t - 200^\circ) \text{ V}$$

Phasor form of voltages

Phase voltages

$$\bar{V}_{RN} = \frac{100 \angle 0^\circ}{\sqrt{2}}$$

$$\bar{V}_{YN} = \frac{100 \angle -120^\circ}{\sqrt{2}}$$

$$\bar{V}_{BN} = \frac{100 \angle -240^\circ}{\sqrt{2}}$$

Line Voltages

$$\bar{V}_{RY} = \frac{173.20 \angle 40^\circ}{\sqrt{2}}$$

$$\bar{V}_{YB} = \frac{173.20 \angle -80^\circ}{\sqrt{2}}$$

$$\bar{V}_{BR} = \frac{173.20 \angle -200^\circ}{\sqrt{2}}$$