

## NOTES Class 50

### Advantages of Three Phase Systems over Single Phase Systems

1. For certain amount of power to be transmitted over certain distance, a three phase system requires less conductor

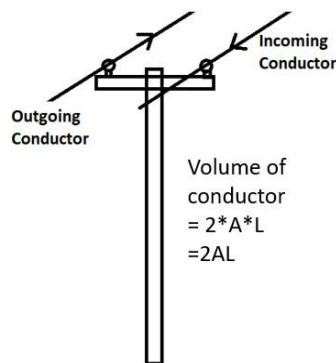


Fig: Single Phase Transmission Line

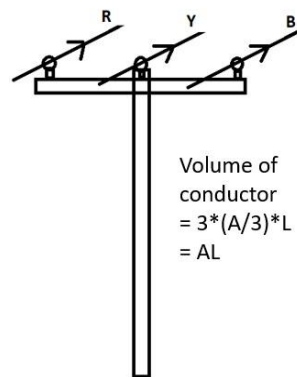


Fig: Three Phase Transmission Line

material compared to single phase system.

2. For the same frame size, a three phase machine can handle higher amount of power compared to its single phase counterpart.
3. Single Phase Power is pulsating in nature, whereas three phase power flowing into a three phase motor is almost constant at every instant. Hence, three phase motors run smoother and less noisy & hence, have better lifespan than a single phase motor.
4. Three Phase Induction Motors are self-starting whereas single phase induction motors are not self-starting in nature which makes three phase induction motors widely popular in

industrial drives.

### Numerical Example on Wattmeter

#### Method Question:

A 3-phase Y-connected, balanced load with a lagging power factor is supplied at 400 V (between the lines). A wattmeter when connected with its current coil in the R-line and voltage coil between R and Y lines gives a reading of 6kW. When the same terminals of the voltage coil are switched over to Y- and B-lines, the current coil connections remaining the same, the reading of the wattmeter remains unchanged. Calculate the line current and power factor of the load. Phase sequence is RYB.


#### Solution:

##### Case 1: CC in R-line and PC between R & Y

lines Wattmeter reading,

$$W_1 = V_{RY} \cdot I_R \cdot \cos(\angle(V_{RY}, I_R))$$
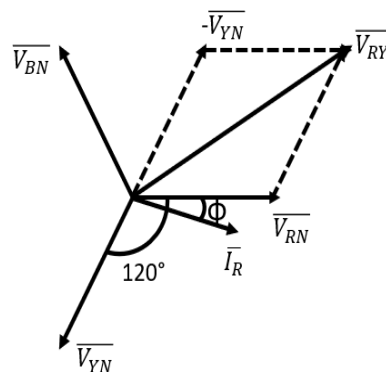
$$\vec{V}_{RY} = \vec{V}_{RN} - \vec{V}_{YN}$$




Therefore,  $W_1 = V_L * I_L * \cos(30 + \phi) = 6000W$

(given) **Case 2: CC in R-line and PC between Y & B**

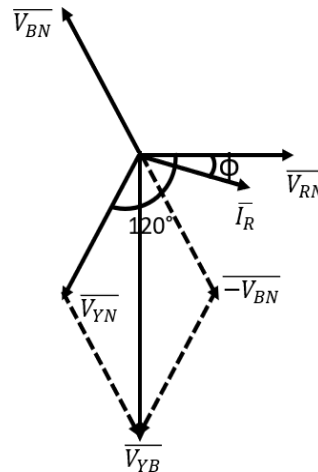**lines Wattmeter reading,**

$$W_2 = V_{YB} * I_R * \cos(\angle(V_{YB}, I_R))$$

$$\vec{V}_{YB} = \vec{V}_{YN} - \vec{V}_{BN}$$



Therefore,  $W_2 = V_L \cdot I_L \cdot \cos(90 - \phi) = 6000W$  (given)

Since it is given that wattmeter reading is same in both the cases,

$$W_1 = W_2$$

$$\text{i.e., } V_L \cdot I_L \cdot \cos(30 + \phi) = V_L \cdot I_L \cdot \cos(90 - \phi)$$

$$\text{Therefore, } \cos(30 + \phi) = \sin \phi$$

$$\text{Hence, } \phi = 30^\circ$$

$$\text{Therefore, Power factor} = \cos \phi = 0.866 \text{ Lag}$$

To find Line current  $I_L$ , substitute  $V_L$  &  $\phi$  values either in  $W_1$  equation or  $W_2$  equation above.

$$\text{Therefore, } W_1 = V_L \cdot I_L \cdot \cos(30 + \phi) =$$

$$6000W \text{ Hence, Line current, } I_L = 30A$$