

## Unit I: Assessment: Assignments

### Assignment – Lecture 4

1. Find the resistance between A&B

