

# ELEMENTS OF ELECTRICAL ENGINEERING

Course Code : UE25EE141A/B

---



## FACULTY CONTRIBUTED:

Department of EEE, RR Campus

Prof . Jyothi T N

Prof. Vadhiraj K P P

Prof. Kruthika N

Prof. Suma S

Prof. Pushpa K R

Prof. Sangeeta Modi

Department of ECE, EC Campus

Prof. Lokesh L

Prof. Dhanashree G Bhate

Dr. Renuka R Kajur

Prof. Rajesh Chandrashekar

Prof. Sangam Kumar G H

# ELEMENTS OF ELECTRICAL ENGINEERING

---




## Numerical Examples – Basic Laws , VDR , CDR

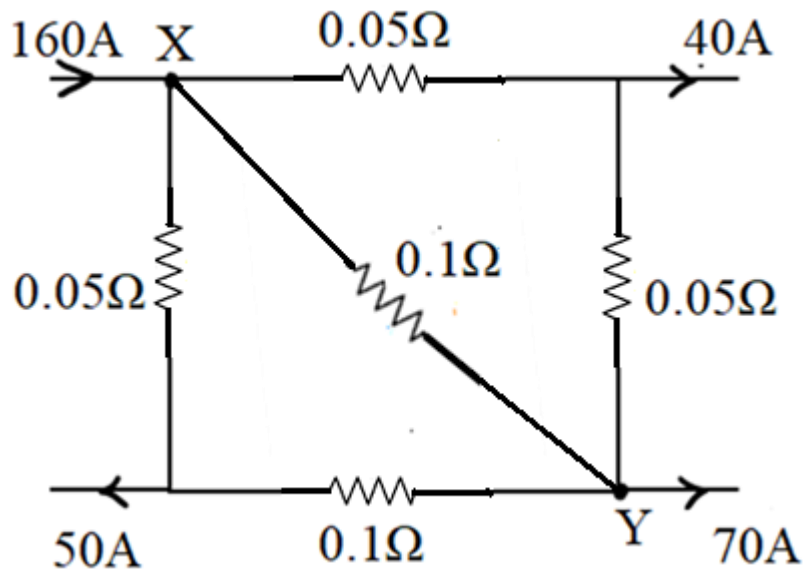**Jyothi T N**

Department of Electrical & Electronics Engineering


By using Kirchhoff's laws, Find current in branch XY for the given circuit.



Solving equation 1 & 2

$$I_1 = 60\text{A}; \quad I_2 = I_{XY} = 40\text{A}$$

**Solution:**

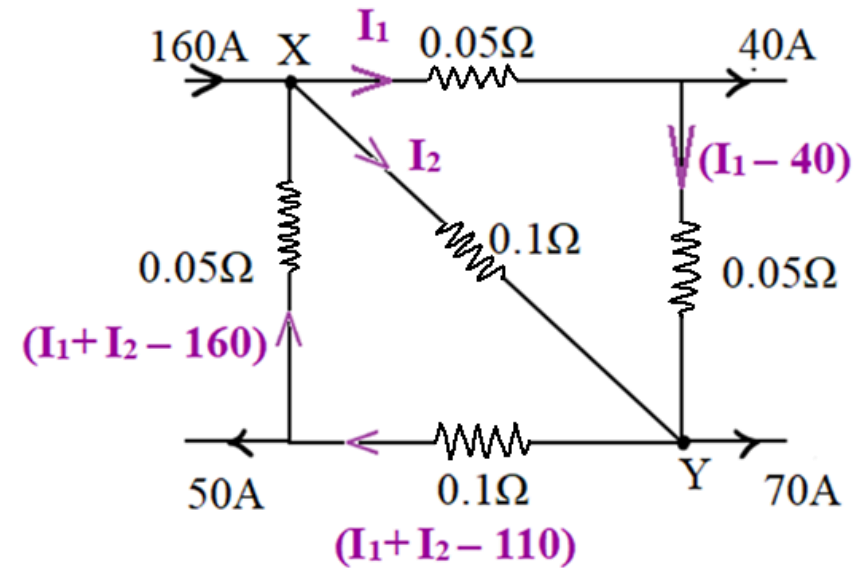


$$-0.05 I_1 - 0.05(I_1 - 40) + 0.1 I_2 = 0$$


$$0.1 I_1 - 0.1 I_2 = 2 \quad \text{-----1}$$

$$-0.1 I_2 - 0.1(I_1 + I_2 - 110) - 0.05(I_1 + I_2 - 160) = 0$$

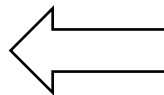
$$0.15 I_1 + 0.25 I_2 = 19 \quad \text{-----2}$$



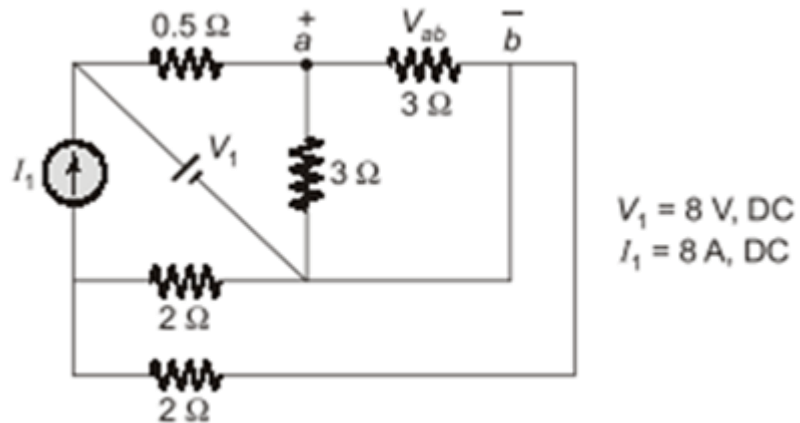For the circuit shown below,  $V_1=8\text{V}$  and  $I_1=8\text{A}$ . Find the voltage  $V_{ab}$




Solution: circuit can be redrawn as

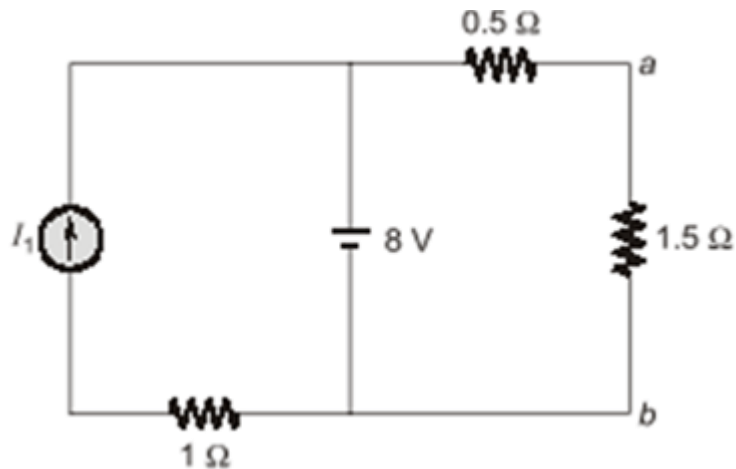

By applying voltage division rule, we can get

$$V_{ab} = 8 \times \frac{1.5}{1.5 + 0.5} = 6\text{ V}$$

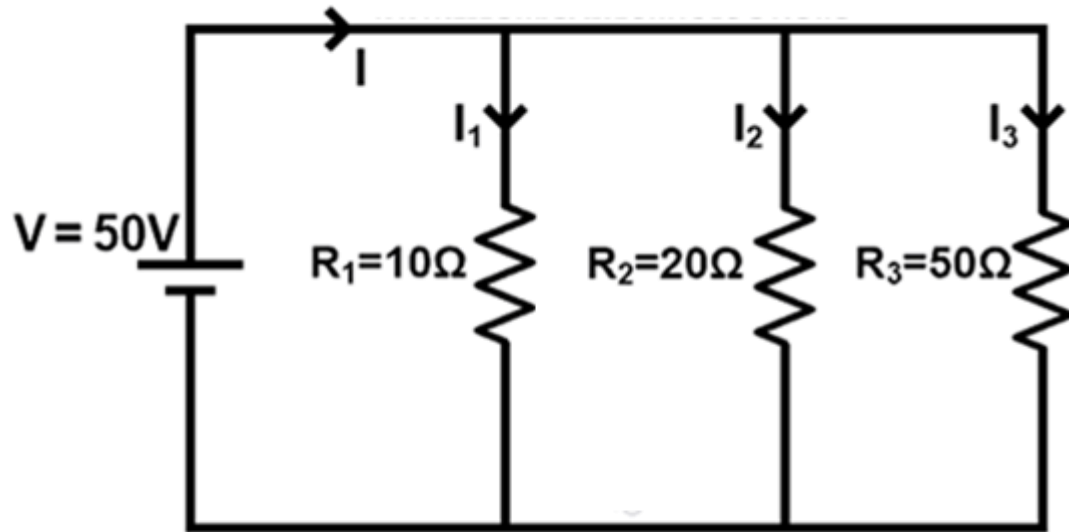Find the current passes through each resistor by the current divider rule for the given network.



### Text Book:

1. “Basic Electrical Engineering” S.K Bhattacharya, 1<sup>st</sup>Edition Pearson India Education Services Pvt. Ltd., 2017
2. “Basic Electrical Engineering”, D. C. Kulshreshta, 2<sup>nd</sup>Edition, McGraw-Hill. 2019
3. “Special Electrical Machines” E G Janardanan, PHI Learning Pvt. Ltd., 2014

### Reference Books:

1. “Engineering Circuit Analysis” William Hayt, Jack Kemmerly, Jamie Phillips and Steven Durbin, 10<sup>th</sup> Edition McGraw Hill, 2023
2. “Electrical and Electronic Technology” E. Hughes (Revised by J. Hiley, K. Brown & I.M Smith), 12<sup>th</sup> Edition, Pearson Education, 2016.



**THANK YOU**

---

**Jyothi T N**

Department of Electrical & Electronics Engineering

**[jyothitn@pes.edu](mailto:jyothitn@pes.edu)**