

ELEMENTS OF ELECTRICAL ENGINEERING

Course Code : UE25EE141A/B



FACULTY CONTRIBUTED:

Department of EEE, RR Campus

Prof . Jyothi T N

Prof. Vadhiraj K P P

Prof. Kruthika N

Prof. Suma S

Prof. Pushpa K R

Prof. Sangeeta Modi

Department of ECE, EC Campus

Prof. Lokesh L

Prof. Dhanashree G Bhate

Dr. Renuka R Kajur

Prof. Rajesh Chandrashekar

Prof. Sangam Kumar G H

ELEMENTS OF ELECTRICAL ENGINEERING

Concept Of Short Circuit, Open Circuit And Numerical

Jyothi T N



Department of Electrical & Electronics Engineering

An Open Circuit has Infinite resistance.




Current through the Open Circuit is Zero.

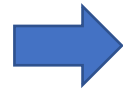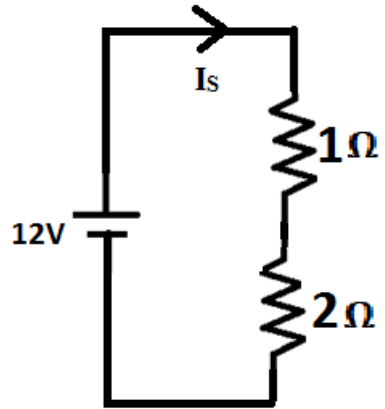Voltage across the Open Circuit can be any finite value.



$$I_S = 4A$$

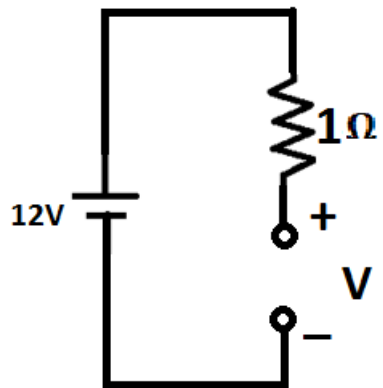

$$I_S = 0A$$
$$V = 12V$$


A Short Circuit has Zero resistance.




Voltage across a Short Circuit is Zero.

Current through the Short Circuit can be any finite value.

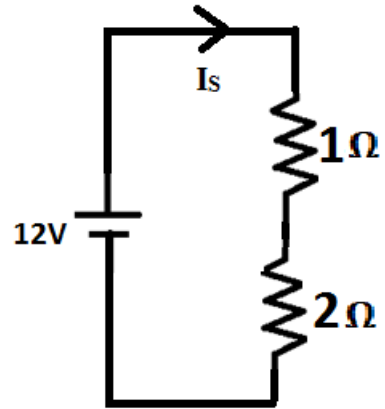Current through a Dead Short Circuit is dangerously high.



$$I_S = 4A$$

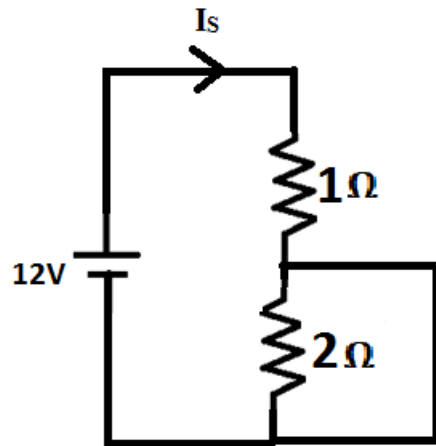

$$I_S = 12A$$


Find the equivalent resistance between X & Y if

i) $R_a = \infty$ & $R_b = \infty$

ii) $R_a = 0$ & $R_b = \infty$


iii) $R_a = \infty$ & $R_b = 0$

iv) $R_a = 0$ & $R_b = 0$

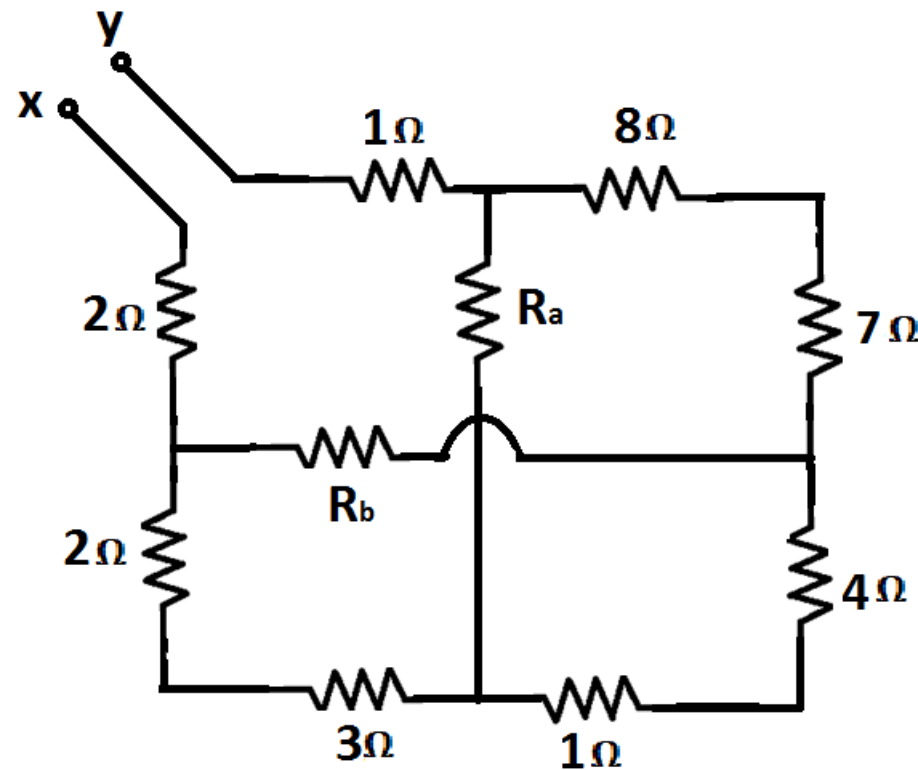

Solution:

Case i) $R_a = \infty$ & $R_b = \infty$

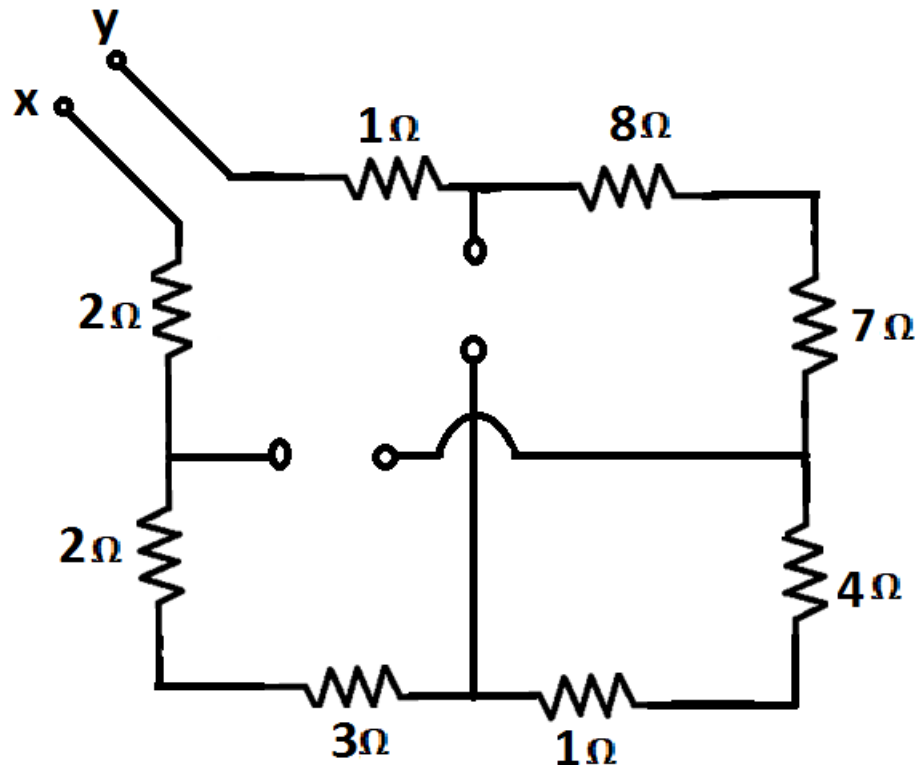


All the resistors are
in series.

Hence, $R_{xy} = 28\Omega$

Solution:



Case ii) $R_a = 0$ & $R_b = \infty$

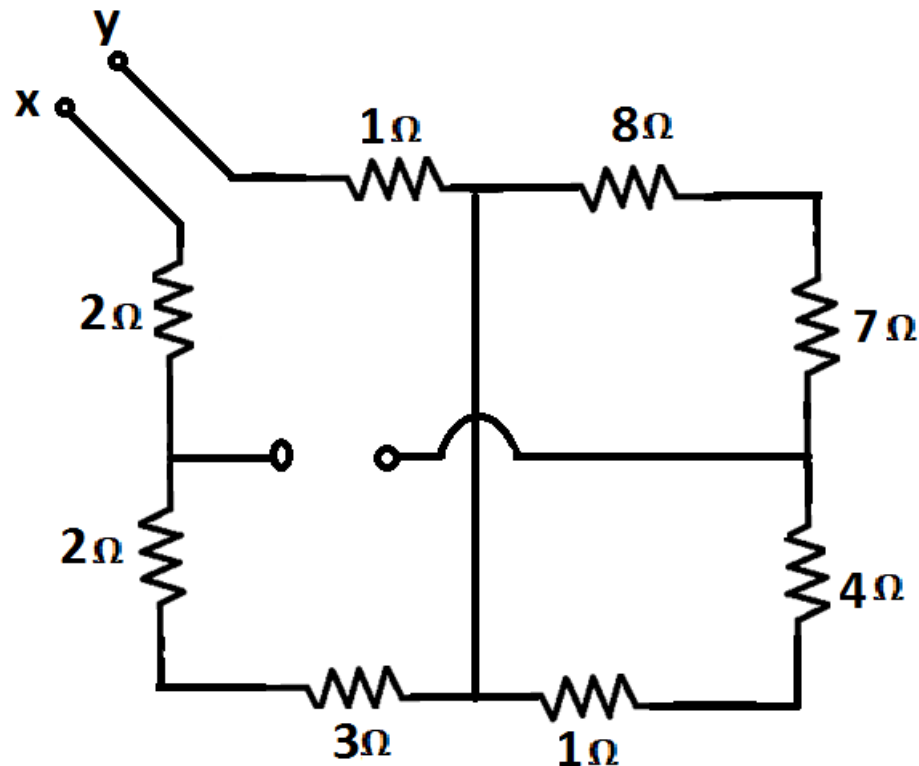

$$R_{XY} = 8\Omega$$

Solution:

Case iv) $R_a = 0$ & $R_b = 0$

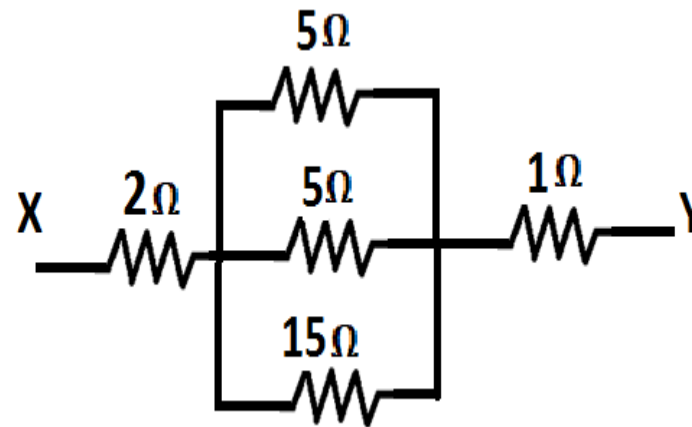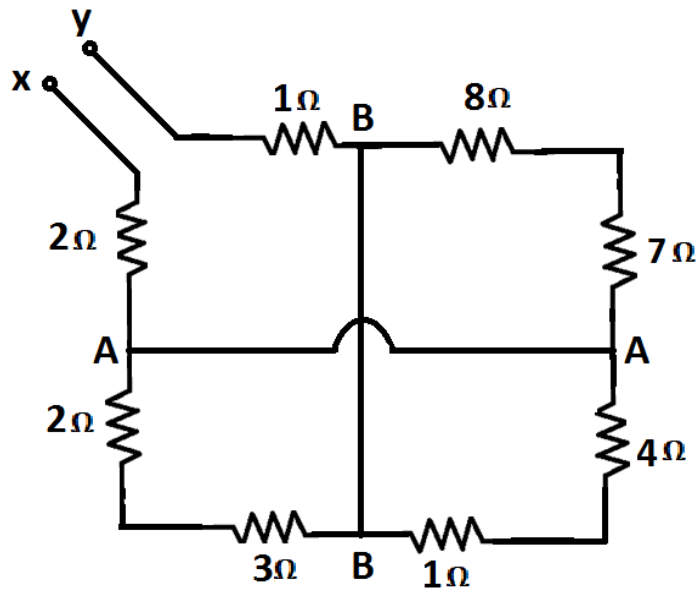

$$R_{XY} = 5.143\Omega$$

Text Book:

1. “Basic Electrical Engineering” S.K Bhattacharya, 1stEdition Pearson India Education Services Pvt. Ltd., 2017
2. “Basic Electrical Engineering”, D. C. Kulshreshta, 2ndEdition, McGraw-Hill. 2019
3. “Special Electrical Machines” E G Janardanan, PHI Learning Pvt. Ltd., 2014

Reference Books:

1. “Engineering Circuit Analysis” William Hayt, Jack Kemmerly, Jamie Phillips and Steven Durbin, 10th Edition McGraw Hill, 2023
2. “Electrical and Electronic Technology” E. Hughes (Revised by J. Hiley, K. Brown & I.M Smith), 12th Edition, Pearson Education, 2016.



THANK YOU

Jyothi T N

Department of Electrical & Electronics Engineering

jyothitn@pes.edu