

## Unit I: Assessment: Assignments

### Assignment – Lecture 13

1. Using Superposition Theorem, Find current through  $4\Omega$  resistor in the network below.

