

Unit I: Assessment: Q & A (Selected)

Lecture 26

Q1. A series RC circuit with  $R = 10 \Omega$ ,  $C = 100 \mu F$  and frequency of 50 Hz obtain expression for the voltage if the current is given by

- (i)  $i = 30 \sin (\omega t)$
- ii)  $I = 30 \sin (\omega t + 45^\circ)$
- (ii)  $i = 3 \sin (\omega t - 60^\circ)$
- (iii)  $i = 3 \sin (\omega t + 30^\circ)$

Solution

$$R = 10 \Omega, C = 100 \mu F$$

$$X_c = 1 / 2 \pi f C = 1 / 2 (3.14) (50) 100 \times 10^{-6}$$

$$= 31.84 \Omega$$

$$Z = 33.36 \Omega$$

$$V_m = I_m \cdot Z$$

$$= 30 (33.36) = 1000 \text{ Volt}$$

$$\Phi = (X_c / R)$$

$$\Phi = 72.55^\circ$$

(i)  $i = 30 \sin (\omega t)$

$$V = 1000 \sin (\omega t - 72.55^\circ)$$

(ii)  $i = 30 \sin (\omega t + 45^\circ)$

$$V = 1000 \sin (\omega t + 45^\circ - 72.55^\circ)$$

$$V = 1000 \sin (\omega t - 27.55^\circ)$$

$$V_m = I_m / Z = 3 (33.36) = 100 \text{ Volt}$$

(iii)  $i = 3 \sin (\omega t - 60^\circ)$

$$V = 100 \sin (\omega t - 60^\circ - 72.55^\circ)$$

$$V = 100 \sin (\omega t - 132.55^\circ)$$

(iv)  $i = 3 \sin (\omega t + 30^\circ)$

$$V = 100 \sin (\omega t + 30^\circ - 72.55^\circ)$$

$$V = 100 \sin (\omega t - 42.55^\circ)$$

## Unit I: Assessment: Q & A (Selected)

PES University