

Unit IV : Assessment Question Bank**Lecture 64****1.**

Derive the condition for maximum efficiency in a single-phase transformer.

2.

A 5 kVA, 1000/200 V, 50 Hz single-phase transformer has the following OC & SC test data:

No-load test conducted at the low-voltage side:

$$W_0 = 90 \text{ W}, I_0 = 1.2 \text{ A}, V_0 = 200 \text{ V}$$

Short-circuit test conducted at the high-voltage side:

$$W_{sc} = 110 \text{ W}, I_{sc} = 5 \text{ A}, V_{sc} = 50 \text{ V}$$

Calculate the efficiency of the transformer at full-load 0.8 p.f. lagging.

PESU