

Unit III: Assessment: Q & A (Selected)

Lecture 46

1. With a neat circuit diagram and phasor diagram, show that two wattmeters are sufficient to measure active power in a three phase system. Also derive an expression for the powerfactor of the system.


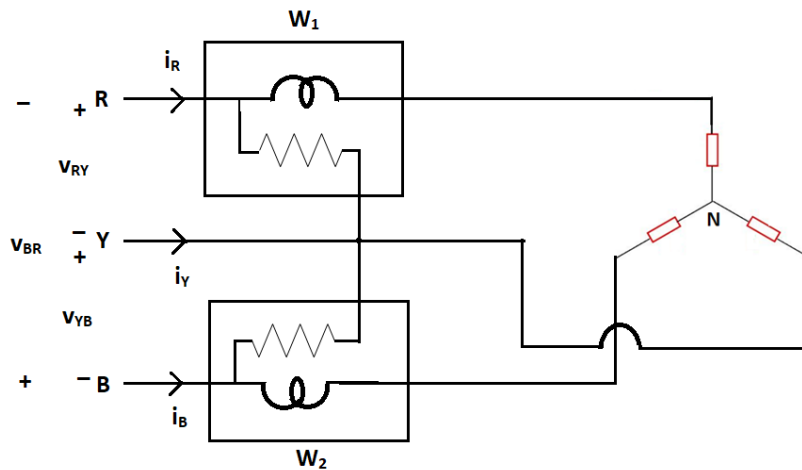


Fig: Two Wattmeter Method circuit diagram

$$W_1 = V_{RY} \cdot I_R \cdot \cos(\angle(V_{RY}, I_R))$$
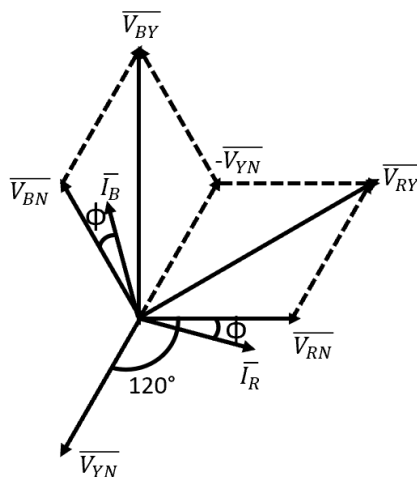
$$W_2 = V_{BY} \cdot I_B \cdot \cos(\angle(V_{BY}, I_B))$$



$$\overline{V_{RY}} = \overline{V_{RN}} - \overline{V_{YN}}$$

$$\overline{V_{BY}} = \overline{V_{BN}} - \overline{V_{YN}}$$

Consider inductive load. Then, phase current lags phase voltage.

$$W_1 = V_{RY} \cdot I_R \cdot \cos(30 + \phi) \quad \& \quad W_2 = V_{BY} \cdot I_B \cdot \cos(30 - \phi)$$

Unit III: Assessment: Q & A (Selected)

$$W_1 = V_{RY} * I_R * \cos(30+\phi) \quad \& \quad W_2 = V_{BY} * I_B * \cos(30-\phi)$$

$$W_1 = V_L * I_L * \cos(30+\phi) \quad \& \quad W_2 = V_L * I_L * \cos(30-\phi)$$

$$\text{Therefore, } W_1 + W_2 = \sqrt{3} * V_L * I_L * \cos\phi = P_{3\text{-phase}} \text{ --- (1)}$$

$$\text{Similarly, } \sqrt{3} * (W_2 - W_1) = \sqrt{3} * V_L * I_L * \sin\phi = Q_{3\text{-phase}} \text{ --- (2)}$$

$$\frac{(2)}{(1)} \rightarrow \frac{Q_{3\text{-phase}}}{P_{3\text{-phase}}} = \frac{\sqrt{3} * (W_2 - W_1)}{W_1 + W_2} = \tan\phi$$

Hence, power factor of the system is,

$$\cos\phi = \cos\left(\tan^{-1}\left(\frac{\sqrt{3} * (W_2 - W_1)}{W_1 + W_2}\right)\right)$$