

UE25EE141A – UNIT 2 – QUESTION BANK – ANSWER KEY

(Unsolved Questions)

Lecture 26

2. $C = 81.27\mu\text{F}$, Current drawn = 5A, PF = 0.45 Lead

Lecture 27

2.

i) PF = 0.99 Lead

ii) Reactive Power in the circuit = -1.22VAR

iii) Magnitude of supply voltage = 8.09V

Lecture 28

1. Resistance of the coil = 19.09Ω

Inductance of the coil = 81mH

Lecture 29

1. Series Equivalent is a Series RL circuit with $R = 1.44\Omega$ and $X_L = 1.92\Omega$

Lecture 32

2. Current supplied = 6.71A; Power = 1.54KW; Power factor = 0.998 Lead

Lecture 33

2. $R = 310\Omega$ & $C = 10\mu F$