

Unit I: Assessment: Assignments

Assignment – Lecture 23

1. A pure inductor of inductance 100mH is connected across an AC supply $100\sin(100\pi t)$ V. Determine
 - i) Inductive Reactance
 - ii) Instantaneous expression for current