

## Unit I: Assessment: Assignments

### Assignment – Lecture 3

**1. Plot the following curves:**

- i) V-I Characteristic of a Practical Voltage Source**
- ii) I-V Characteristic of a Practical Current Source**