

Unit III: Assessment: Q & A (Selected)

Lecture 47

1. Discuss in brief how wattmeter readings vary

- i) when pf of the load is unity
- ii) when pf of the load is > 0.5
- iii) when pf of the load = 0.5
- iv) when pf of the load is < 0.5

Solution:

Phase Angle, ϕ	Load Power factor, $\cos\phi$	$W_1 = V_L I_L \cos(30+\phi)$	$W_2 = V_L I_L \cos(30-\phi)$	Comments
0°	1	$\frac{\sqrt{3}V_L I_L}{2}$	$\frac{\sqrt{3}V_L I_L}{2}$	$W_1 = W_2$
30°	0.866 Lag	$\frac{V_L I_L}{2}$	$V_L I_L$	$W_1 = \frac{W_2}{2}$
60°	0.5 Lag	0	$\frac{\sqrt{3}V_L I_L}{2}$	$W_1 = 0;$ $W_2 = P_{3\text{-phase}}$
$>60^\circ$	< 0.5 Lag	Negative	Positive	$W_1 = \text{-ve};$ $W_2 = \text{+ve}$

Unit III: Assessment: Q & A (Selected)

PES University