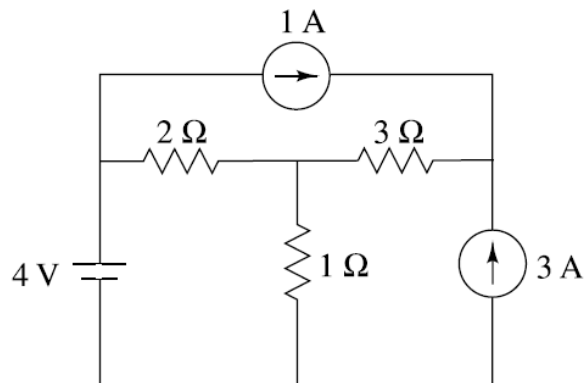


## Unit I: Assessment Question Bank

### Lecture 14

1. State Thevenin's Theorem. Draw Thevenin's Equivalent network.
2. Find the current through the  $1\ \Omega$  resistor using Thevenin's Theorem.



PESU