

Unit I: Assessment Question Bank**Lecture 25**

1. A choke coil is connected to a 240V AC supply. When the frequency of the supply is 50Hz, an ammeter connected in series with the choke reads 60A. On increasing the frequency of the supply to 100Hz, the same ammeter reads 40A. Calculate r and L of the coil.

PES University