

## Unit I: Assessment: Assignments

### Assignment – Lecture 14

1. Using Thevenin's Theorem, find the range of voltage across  $R_L$  as it varies from  $10\text{K}\Omega$  to  $20\text{K}\Omega$ .

