

Unit III: Assessment Question Bank

Lecture 41

1. A balanced, three-phase, star-connected load of 100 kW takes a leading current of 80 A, when connected across a three-phase, 1100-V, 50-Hz supply. Find the circuit constants of the load per phase.

[ANS: $R = 5.21 \, \Omega$, $C = 531.25 \, \mu\text{F}$]

2. A balanced three-phase star-connected load of $(8 + j6) \, \Omega$ per phase is supplied by a 400 V, 50 Hz supply. Calculate the line current, power factor, active, and reactive power.

[ANS: $I_L = 23.09 \text{ A}$, $\cos \phi = 0.8$ Lag, $P = 12.79 \text{ KW}$, $Q = 9.59 \text{ KVAR}$]