

UE25EC141A - Electronic Principles and Devices (4-0-0-4-4)**Unit3: Assignment**

- 1) With a neat diagram explain Common base input- output characteristics (6 Marks)
- 2) With a neat diagram explain Common emitter input-output characteristics. (6 Marks)
- 3) Obtain the relationship between α and β (4 Marks)
- 4) Explain briefly operating point. (6 Marks) and Write a note on effects of temperature on Q-point (4 Marks)
- 5) With mathematical interpretations explain Fixed bias configuration (6 Marks)
- 6) With mathematical interpretations explain Emitter bias configuration (6 Marks)
- 7) Explain with mathematical interpretations Voltage divider bias configuration (7 Marks)
- 8) Explain Single Stage CE Amplifier. (6 Marks)
- 9) With a neat diagram explain the Common Mode operation in Operational Amplifier [Op-Amp] (4 Marks)
- 10) Define the following with respect to Op-Amps (8 Marks)
 - (i) Input offset Voltage
 - (ii) Output offset Voltage
 - (iii) Input resistance
 - (iv) Output resistance
- 11) Define the following with respect to op-amp (4 Marks)
 - (i) Slew rate
 - (ii) Common mode rejection ratio
- 12) Explain the Virtual Ground concept. (4 Marks) With relevant mathematical interpretation explain an Op-Amp inverting amplifier.(4 Marks) With relevant mathematical interpretation explain an Op-Amp Non-inverting amplifier. (4 Marks)
- 13) With relevant mathematical interpretation explain an Op-Amp summing amplifier. (4 Marks)
- 14) With relevant mathematical interpretation explain an Op-Amp sub tractor. (4 Marks)
- 15) Explain unity follower or voltage follower using Op-Amp (4 Marks)