

ELEMENTS OF ELECTRICAL ENGINEERING

Course Code : UE25EE141A/B



FACULTY CONTRIBUTED:

Department of EEE, RR Campus

Prof . Jyothi T N
Prof. Vadhiraj K P P
Prof. Kruthika N
Prof. Suma S
Prof. Pushpa K R
Prof. Sangeeta Modi

Department of ECE, EC Campus

Prof. Lokesh L
Prof. Dhanashree G Bhate
Dr. Renuka R Kajur
Prof. Rajesh Chandrashekar
Prof. Sangam Kumar G H


ELEMENTS OF ELECTRICAL ENGINEERING

Analysis of Single-Phase AC circuits with R Load , L Load and C Load

Jyothi T N

Department of Electrical & Electronics Engineering

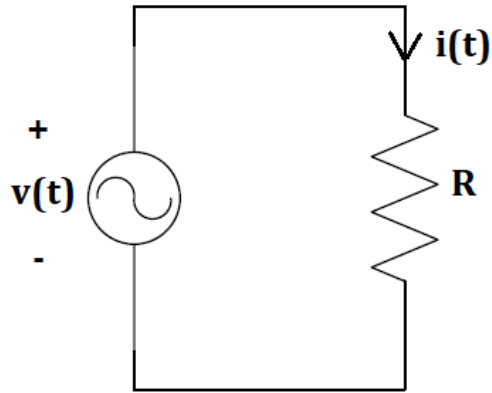Response of Resistive Load to Sinusoidal Supply



Let the supply voltage be $v(t) = V_m \sin(\omega t)$

where, V_m is the peak value of voltage


By Ohm's Law, $i(t) = \frac{v(t)}{R}$

Hence current will be of the form, $i(t) = I_m \sin(\omega t)$

where, $I_m = \frac{V_m}{R}$ is the peak value of current

ELEMENTS OF ELECTRICAL ENGINEERING

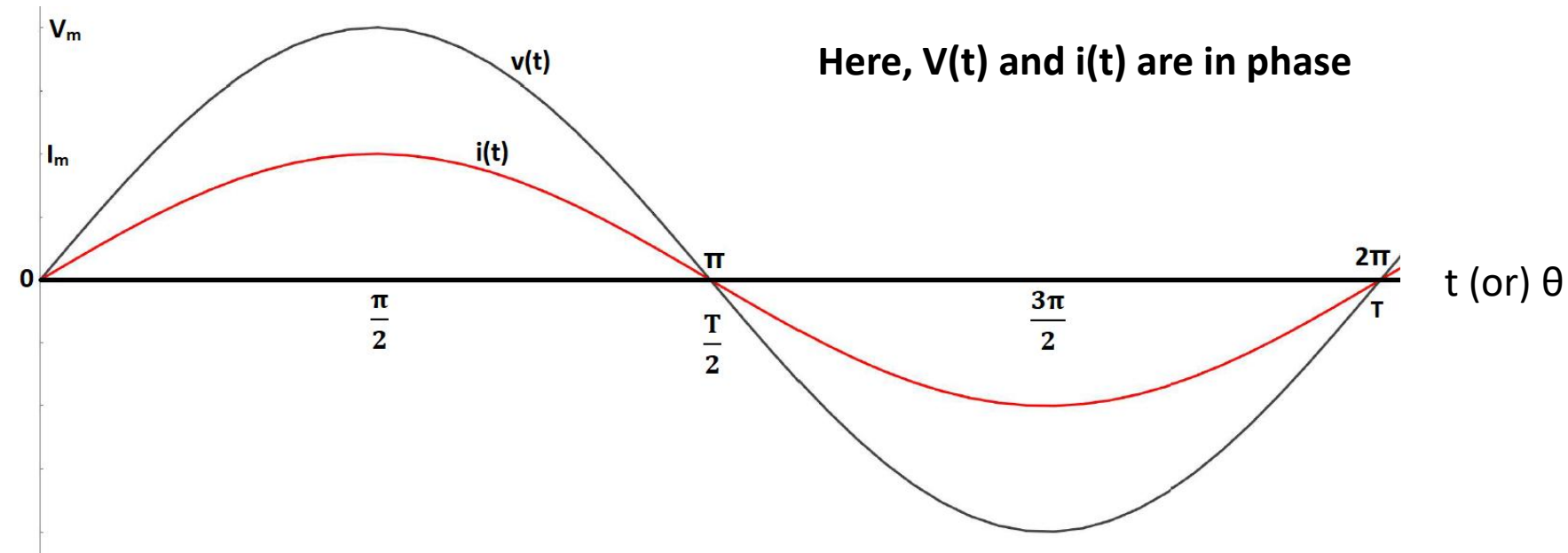Response of Resistive Load to Sinusoidal Supply



$$v(t) = V_m \sin(\omega t) \Rightarrow \bar{V} = \frac{V_m}{\sqrt{2}} \angle 0^\circ$$


$$i(t) = I_m \sin(\omega t) \Rightarrow \bar{I} = \frac{I_m}{\sqrt{2}} \angle 0^\circ$$

Phasor Diagram:



$$\text{Impedance, } Z = \frac{\bar{V}}{\bar{I}} = R \angle 0^\circ = R \, \Omega$$

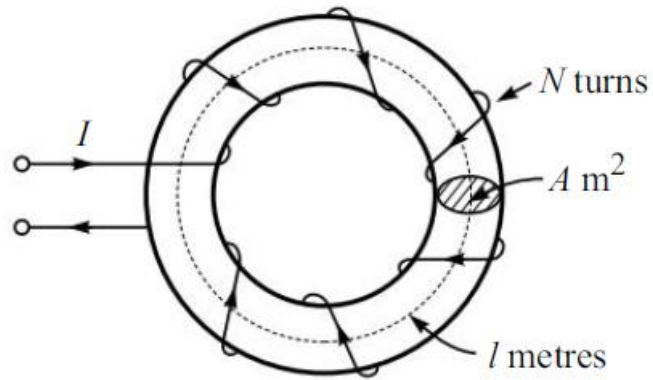An inductor is obtained by winding the conductor into a coil.



A current carrying coil sets up a magnetic field around it.

Magnetic field is expressed as magnetic flux ϕ around the coil.

$$\text{Magnetic flux } \phi = \frac{\text{Magnetomotive Force}}{\text{Reluctance}} = \frac{N \cdot I}{S}$$

$$\text{Where, } S = \text{Reluctance} = \frac{\text{length}}{(\text{Permeability} \cdot \text{Area})}$$

Magnetic flux, ϕ is directly proportional to the current in the inductor coil.

i.e., $\phi \propto i$

i.e., $N\phi \propto i$

Where, $N\phi$ is called **flux linkages** denoted by ψ

Therefore, ψ is proportional to i


$$\Rightarrow \psi = Li$$

Where, L is the proportionality constant called 'Inductance' of the inductor.

$$L = \frac{\psi}{i} = \frac{N\phi}{i}$$

Inductance is measured in Henrys (H)

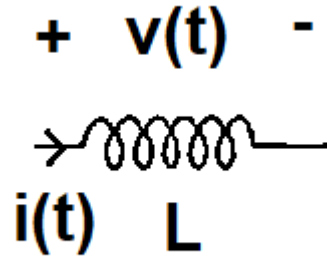Voltage – Current relationship in an inductor



The voltage across the terminals of an inductor is directly proportional to rate of change of flux linkages.

$$\text{i.e., } v(t) \propto \frac{d}{dt}(\psi)$$


$$v(t) = \frac{d}{dt}(\psi) = \frac{d}{dt}(N\phi) = N \frac{d\phi}{dt} = \frac{d}{dt}(Li) = L \frac{di}{dt}$$

$$\text{i.e., voltage } v(t) \text{ is related to current } i(t) \text{ as } v(t) = L \frac{di(t)}{dt}$$

Therefore, $i(t)$ can be expressed as

$$i(t) = \frac{1}{L} \int v(t) dt$$

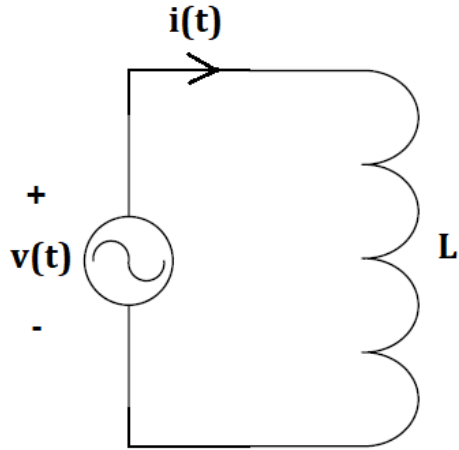Response of Pure Inductive Load to Sinusoidal Supply



Let the supply voltage be $v(t) = V_m \sin(\omega t)$


In a pure inductor, $i(t) = \frac{1}{L} \int v(t) dt$

$$= \frac{-V_m}{\omega L} \cos(\omega t)$$

$$= I_m \sin(\omega t - 90^\circ)$$

where, $I_m = \frac{V_m}{\omega L}$ is the peak value of current

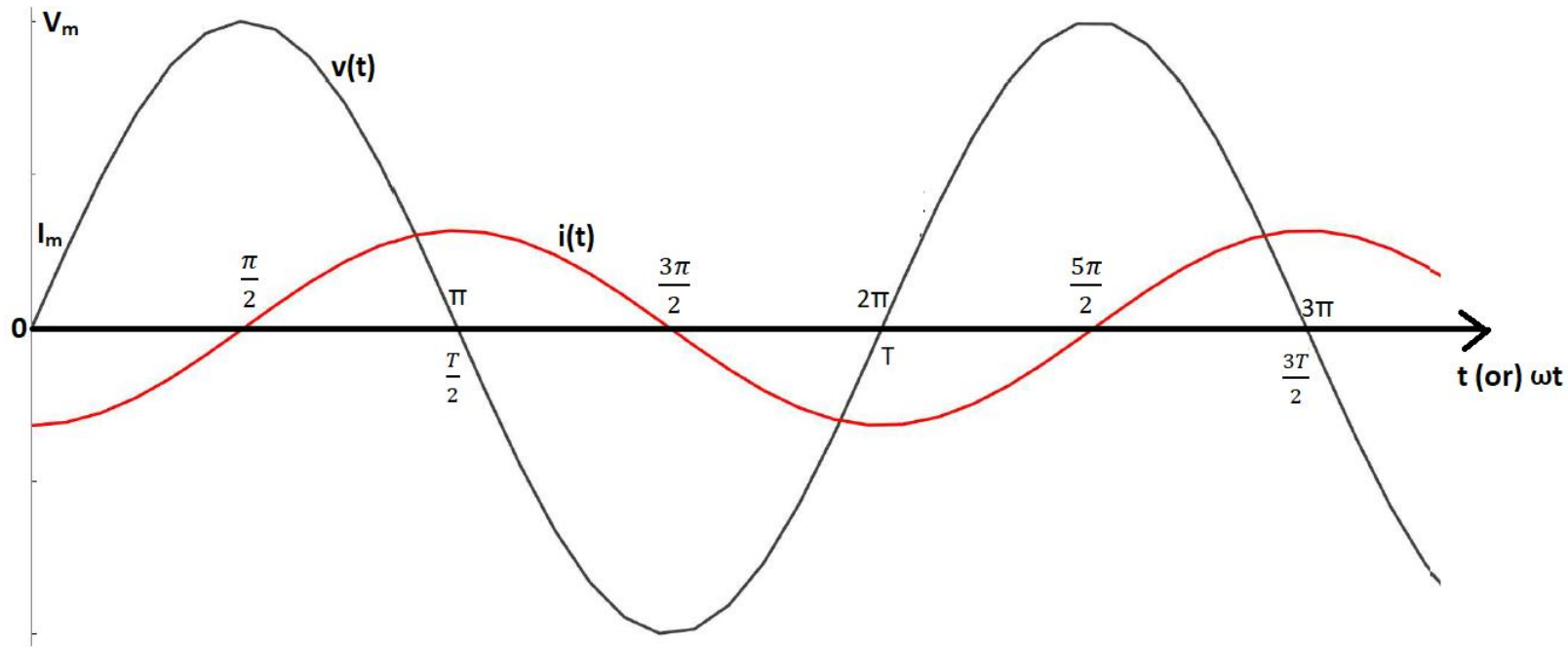Response of Pure Inductive Load to Sinusoidal Supply



In a pure inductor, current **lags** voltage by 90°


ELEMENTS OF ELECTRICAL ENGINEERING

Response of Pure Inductive Load to Sinusoidal Supply

$$v(t) = V_m \sin(\omega t) \Rightarrow \bar{V} = \frac{V_m}{\sqrt{2}} \angle 0^\circ$$

$$i(t) = I_m \sin(\omega t - 90^\circ) \Rightarrow \bar{I} = \frac{I_m}{\sqrt{2}} \angle -90^\circ$$


Phasor Diagram:

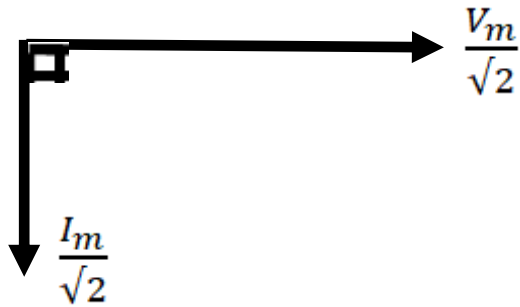

$$Z = \frac{\bar{V}}{\bar{I}} = \frac{\frac{V_m}{\sqrt{2}} \angle 0^\circ}{\frac{I_m}{\sqrt{2}} \angle -90^\circ} = \omega L \angle 90^\circ = jX_L \quad \Omega$$

Where, $X_L = \omega L$ is called '**Inductive Reactance**'

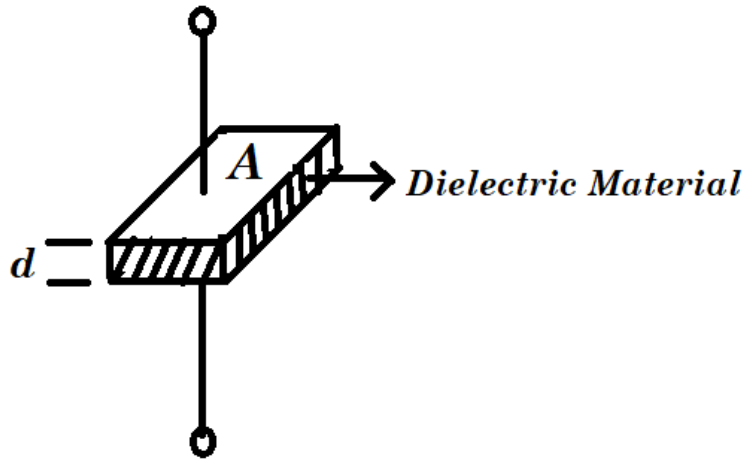A Capacitor is obtained by placing a dielectric medium between the conducting plates.




$$\text{Capacitance, } C = \frac{\epsilon A}{d} \text{ Farad}$$

Where, A is the area of each of the plates in m^2

d is the distance between the plates in m

ϵ is the permittivity of the dielectric medium in F/m

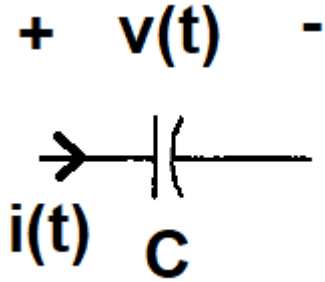Voltage – Current relationship in a Capacitor



The charge on the plates of a capacitor is directly proportional to the voltage across its terminals.

$$\text{i.e., } q(t) \propto v(t) \Rightarrow q(t) = Cv(t)$$


The constant of proportionality 'C' is called Capacitance of the Capacitor.

$$\text{Hence, current, } i(t) = \frac{dq(t)}{dt} = C \frac{dv(t)}{dt}$$

Therefore, $v(t)$ can be expressed as

$$v(t) = \frac{1}{C} \int i(t) dt$$

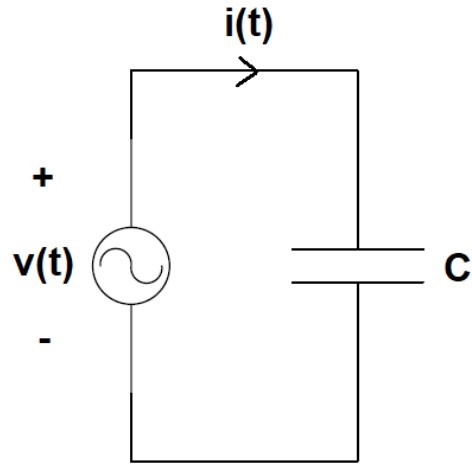Response of Pure Capacitor to Sinusoidal Supply




Let the supply voltage be $v(t) = V_m \sin(\omega t)$

$$\begin{aligned}\text{In a pure capacitor, } i(t) &= C \frac{dv(t)}{dt} \\ &= CV_m \omega \cos(\omega t) \\ &= I_m \sin(\omega t + 90^\circ)\end{aligned}$$

Where, $I_m = V_m \omega C$ is the peak value of current

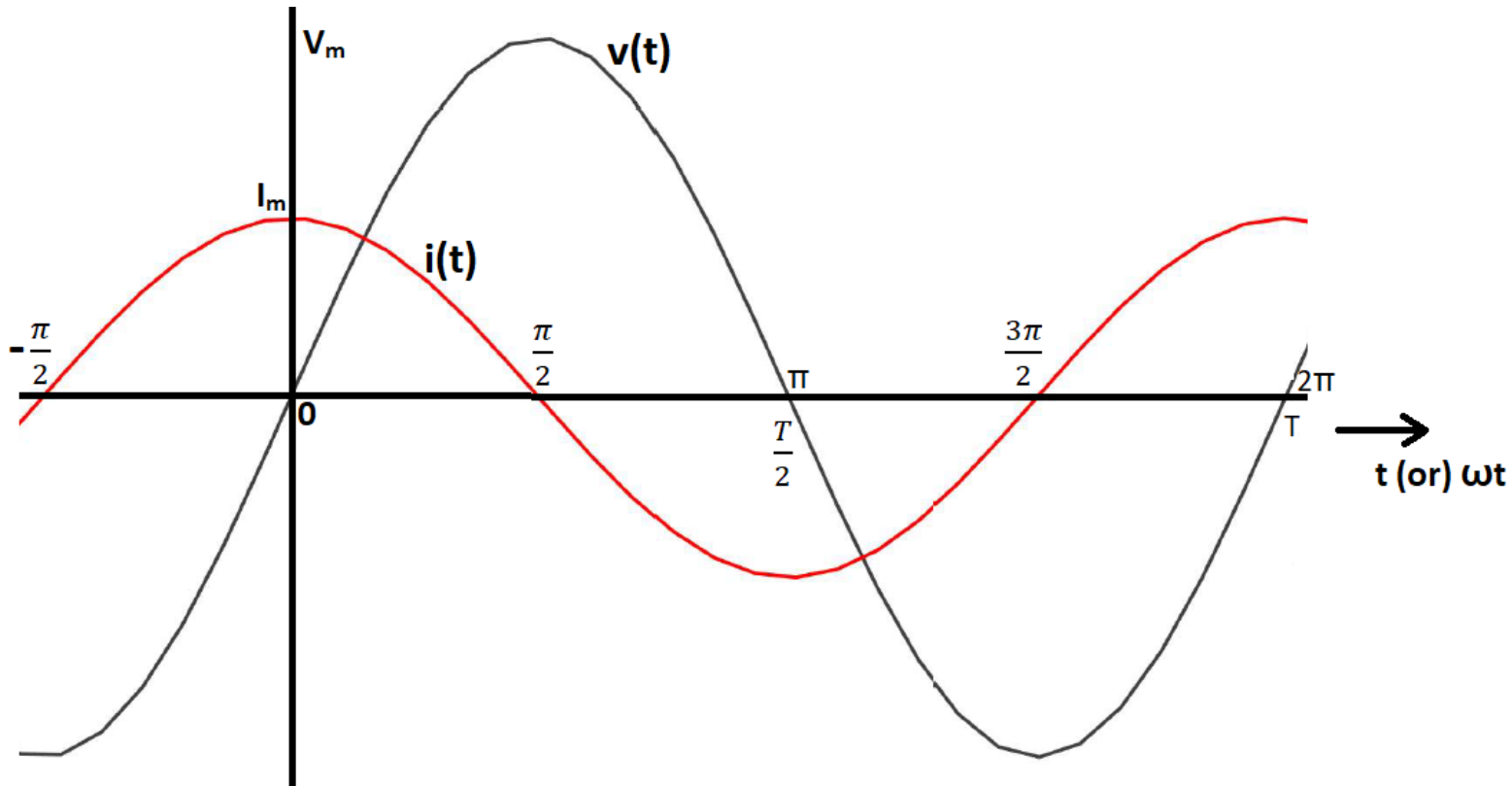Response of Pure Capacitor to Sinusoidal Supply



In a pure capacitor, current **leads** voltage by 90°


ELEMENTS OF ELECTRICAL ENGINEERING

Response of Pure Capacitor to Sinusoidal Supply

$$v(t) = V_m \sin(\omega t) \Rightarrow \bar{V} = \frac{V_m}{\sqrt{2}} \angle 0^\circ$$

$$i(t) = I_m \sin(\omega t + 90^\circ) \Rightarrow \bar{I} = \frac{I_m}{\sqrt{2}} \angle 90^\circ$$

Phasor Diagram:

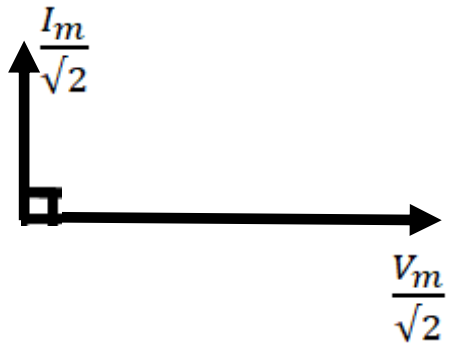

$$Z = \frac{\bar{V}}{\bar{I}} = \frac{\frac{V_m}{\sqrt{2}} \angle 0^\circ}{\frac{I_m}{\sqrt{2}} \angle 90^\circ} = \frac{1}{\omega C} \angle -90^\circ = -jX_c \quad \Omega$$

Where, $X_c = \frac{1}{\omega C}$ is called '**Capacitive Reactance**'

Text Book:

1. “Basic Electrical Engineering” S.K Bhattacharya, 1stEdition Pearson India Education Services Pvt. Ltd., 2017
2. “Basic Electrical Engineering”, D. C. Kulshreshta, 2ndEdition, McGraw-Hill. 2019
3. “Special Electrical Machines” E G Janardanan, PHI Learning Pvt. Ltd., 2014

Reference Books:

1. “Engineering Circuit Analysis” William Hayt, Jack Kemmerly, Jamie Phillips and Steven Durbin, 10th Edition McGraw Hill, 2023
2. “Electrical and Electronic Technology” E. Hughes (Revised by J. Hiley, K. Brown & I.M Smith), 12th Edition, Pearson Education, 2016.



THANK YOU

Jyothi T.N

Department of Electrical & Electronics Engineering
jyothitn@pes.edu