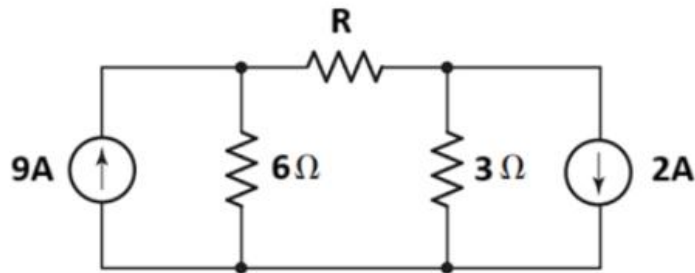


Unit I: DC Circuits

Notes Class - 16

Example: In the given network, apply Thevenin's Theorem and determine the range of current through R as it varies between 1Ω and 10Ω



ii)

Finding V_{TH} :

Removing Load resistance R , an open circuit is created.

Voltage across the open circuit, $V_{TH} = 9 \times 6 + 3 \times 2 = 60V$

Finding R_{TH} :

Removing R and replacing both current sources with open circuit,

$R_{TH} = 6\Omega$ and 3Ω in series $= 9\Omega$

Finding Load current range:

$$I_L = \frac{V_{TH}}{R_{TH} + R_L}$$

When $R = 1\Omega$, $I_L = 6A$

When $R = 10\Omega$, $I_L = 3.15A$

Hence range of current $= 3.15A$ to $6A$