

### Unit III: Assessment: Assignments

---

#### Assignment Class 42

1. It is observed that first line current in a balanced delta system is  $20\sin(\omega t + 30^\circ)$  A. Express all the three phase currents and all the three line currents in both time form and phasor form.