

Unit I: Assessment: Assignments

Assignment – Lecture 10

1. Explain by an example, the difference between Loop & Mesh
2. Find the current through 4Ω resistor in the network shown using Mesh Analysis.

