

Unit I: Assessment Question Bank**Lecture 12**

1. State and explain Superposition Theorem.
2. Find the current through 1Ω resistor in the circuit shown

