

**PES UNIVERSITY**  
**Dept. of Electronics and Communication Engineering      2025**

**UE25EC141A - Electronic Principles and Devices (4-0-0-4-4)**  
**Assignment Questions**

<b>UNIT III: DIGITAL ELECTRONICS</b>	
<b>Class 1</b>	
1.	Define Universal Gates. List the difference between Basic Gates and Universal Gates with examples
<b>Class 2</b>	
2.	Write the Truth Table Considering X,Y and Z as inputs to state distributive Property for Boolean Algebra
<b>Class 3</b>	
3.	Get the Standard SOP for Logical Expression $Y = (A+B')(A'+C')(A'+B')$ and define the function for the expression.
<b>Class 4</b>	
4.	Realize 3 input XOR gate using i. 2 input NAND gates ii. 2 input NOR gates
<b>Class 5</b>	
5.	Simplify and Realize $Y = (A'B + A' + AB)'$ using Universal NAND Gate
<b>Class 6</b>	
6.	Simplify the following Boolean expression $Y = ((A+B'C)(A'+B'+C')(A'+B))'$
<b>Class 7</b>	
7.	Write the Truth table and logic expressions for Sum and Carry of a (i) Half adder (ii) Full adder
<b>Class 9</b>	
8.	What are sequential circuits? <sup>iv</sup> Mention the key features of sequential circuits.
<b>Class 10</b>	
9.	With the help of logic diagram and characteristic table discuss the working of JK flip-flop.
<b>Class 11</b>	
10.	With the help of logic diagram and table discuss the working of 3 – bit asynchronous down counter.
<b>Class 12</b>	
11.	With the help of logic diagram and table discuss the working of 4 – bit SISO shift register with data initially at “0000” with “1011” to be loaded. Also find the contents of shift register after 5 clock pulses.