

UE25EE141A – UNIT 1 – QUESTION BANK – ANSWER KEY

Lecture 1

2. 26V

Lecture 2

1. 240Ω

2. $V_1 = V_2 = 9.412V$

Power dissipated in $2k\Omega$ resistor is $41.78mW$

Power dissipated in $4k\Omega$ resistor is $20.89mW$

Power dissipated in $8k\Omega$ resistor is $10.44mW$

Lecture 3

2. $i_{out} = 8.75mA$

Lecture 4

1. $R_1 = 1.43\Omega$

$R_2 = 0.57\Omega$

$R_3 = 2\Omega$

Lecture 5

1. Current through Ammeter A would be $12A$

Current through Ammeter B would be $8A$

2. $V_{AB} = 77V$ with S Closed; $V_{AB} = 105V$ with S Open

Lecture 6

1. Current through branch AB is 1A

Lecture 7

2. Equivalent Star is $R_a = 0.5\Omega$, $R_b = 0.33\Omega$ & $R_c = 1\Omega$
3. Equivalent Delta is $R_{ab} = 3.67\Omega$, $R_{bc} = 11\Omega$ & $R_{ca} = 5.5\Omega$

Lecture 8

1. $R_{AB} = 9.65\Omega$
2. $R_{AB} = 6.31\Omega$

Lecture 9

1. $R_{AB} = 24.83\Omega$
2. $R_{AB} = 29.765\Omega$

Lecture 10

1. $I_1 = 0.66 \text{ A}$, $I_2 = 0.24 \text{ A}$ & $I_3 = 0.26 \text{ A}$

Hence, Current supplied by the battery = 0.66 A

2.

$$I_1 = 6.01 \text{ A}$$
$$I_2 = 3.27 \text{ A}$$
$$I_3 = 3.38 \text{ A}$$
$$I_{5\Omega} = 3.38 \text{ A}$$

Lecture 11

1. $I_1 = 6 \text{ A}$, $I_2 = 7 \text{ A}$ & $I_3 = 3 \text{ A}$

Hence, Current through 3Ω resistor = 3 A

2. $I_1 = 1.833 \text{ A}$, $I_2 = -1.166 \text{ A}$ & $I_3 = -8 \text{ A}$

Hence, Current through 6Ω resistor = 2.999 A

Lecture 12

Q2. Current due to 4V battery acting alone in 1Ω is 1.33A

Current due to 3A source acting alone in 1Ω is 2A

Current due to 1A source acting alone in 1Ω is 0.67A

Hence, by SPT, Total current $I = I' + I'' + I''' = 4\text{A}$

Lecture 13

1. Voltage across 7Ω resistor when 7A source acting alone is 18.052V

Voltage across 7Ω resistor when 2A source acting alone is 3.68V

Hence, by SPT, Voltage across 7Ω resistor, $V = V' + V'' = 21.73\text{V}$

2. Voltage across A&B when 6V battery acting alone is 6V

Voltage across A&B when 5A source is acting alone is 0V

Voltage across A&B when 10V battery acting alone is 10V

Hence, by SPT, Voltage across A&B, $V = V' + V'' + V''' = 16\text{V}$

Lecture 14

Q2. $V_{TH} = 12V$; $R_{TH} = 2\Omega$

Hence, current through 1Ω resistor = $4A$

Lecture 15

1. $V_{TH} = 1V$; $R_{TH} = 2.75\Omega$

Lecture 16

1. $V_{TH} = 4V$; $R_{TH} = 6\Omega$