

Unit I: Assessment Question Bank**Lecture 4**

1. In the circuit shown, current in the network is 50 A & 70 A when the switch is in position 1 and 2 respectively and 25 A with switch open. Find the value of resistors.

