

Unit I: Assessment Question Bank

Lecture 1

1. Define

- i) Electric current, Potential Difference & Electric Power
- ii) KCL & KVL
- iii) Active & Passive Elements & Sign conventions

2. Find the voltage V_{AB} in the network shown:

(Ans : 26V)

