

Unit I: Assessment: Assignments

Assignment – Lecture 34

1. Explain with the help of a phasor diagram how connecting a capacitor in parallel with lagging load improves overall powerfactor of the system.