

Unit I: Assessment Question Bank**Lecture – 31**

1. A parallel RC Circuit is connected across 200V, 50 Hz supply. If the supply current and current in resistor are 10A & 6A respectively, determine
 - i) Current in capacitor
 - ii) Values of R & C
 - iii) Active, Reactive and Apparent Powers supplied by the source.
 - iv) Powerfactor of the network

PES University