

Lecture 28

2. The admittance of a circuit is $(0.05-j0.08)S$. Find the values of the resistance and inductive reactance of the circuit if they are a) in parallel b) in series.

Solution:

(i) parallel.

$$Y = 0.05 - j0.08$$


Compare with $Y = G - jB_L$

$$G = 0.05$$

$$R = \frac{1}{G} = 20 \Omega$$

$$B_L = 0.08$$

$$X_L = \frac{1}{B_L} = 12.6 \Omega$$

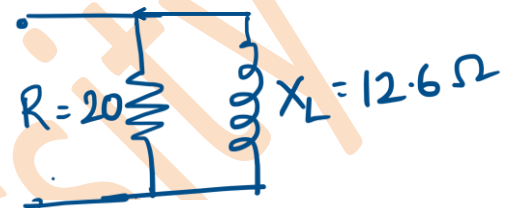

(ii) Series

$$Z = \frac{1}{Y} = \frac{1}{0.05 - j0.08} = 5.62 + j8.98$$

$$R = 5.62$$

$$X_L = 8.98$$

