


Unit I: DC Circuits

Notes Class- 15

Numerical Example on Thevenin's Theorem:


Numerical Example 1:

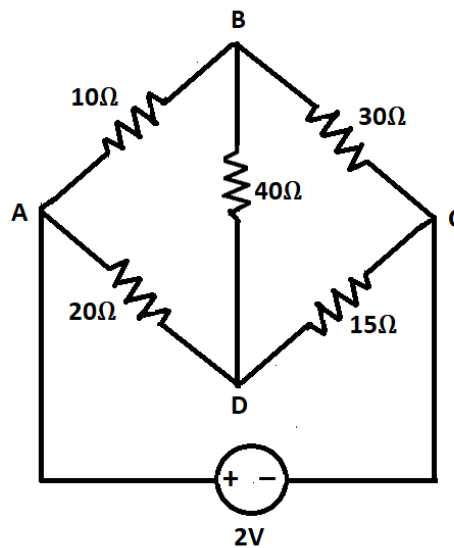Using Thevenin's Theorem, find the magnitude and direction of current in the branch BD in the network shown.



Solution:

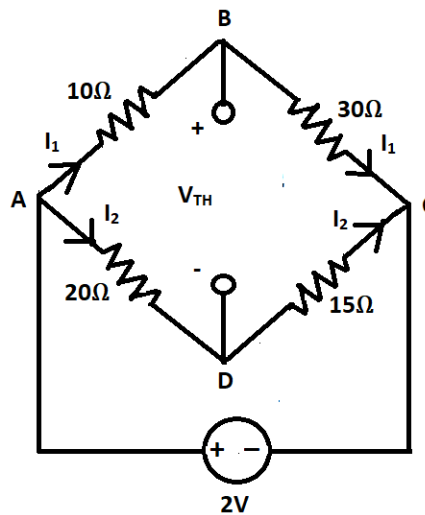Finding V_{TH} : Here 40Ω resistor is the load resistor.



Here, 10Ω and 30Ω are in series. Hence, $I_1 = \frac{2V}{40\Omega} = 0.05A$


Unit I: DC Circuits

Also, 20Ω and 15Ω are in series. Hence, $I_2 = \frac{2V}{35\Omega} = 0.057A$


By KVL (ACDA), $-10 \cdot I_1 - V_{TH} + 20 \cdot I_2 = 0$

Hence, $V_{TH} = 0.64V$

Finding R_{TH} :

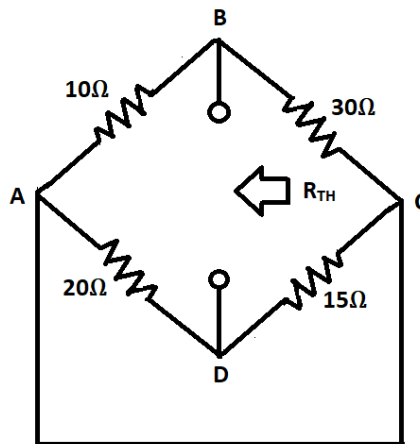


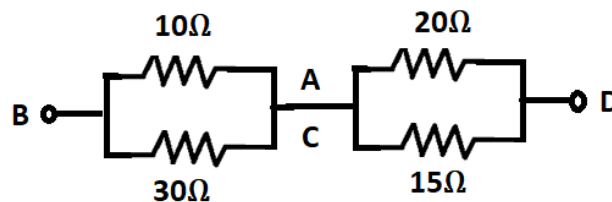The above network can be rearranged as follows:



Hence, $R_{TH} = (10\Omega \parallel 30\Omega) + (20\Omega \parallel 15\Omega) = 16.07\Omega$.

Thevenin's Equivalent Circuit:

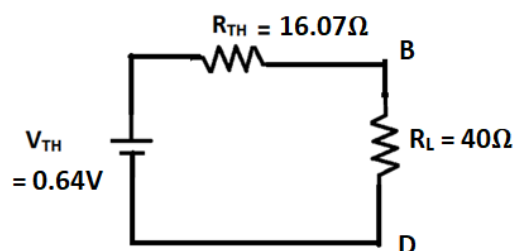


$$\text{Load current } I_L = \frac{V_{TH}}{R_{TH} + R}$$

Hence, current through the branch BD is 11.41mA and flows from terminal B to terminal D.

Unit I: DC Circuits

Numerical Example 2:

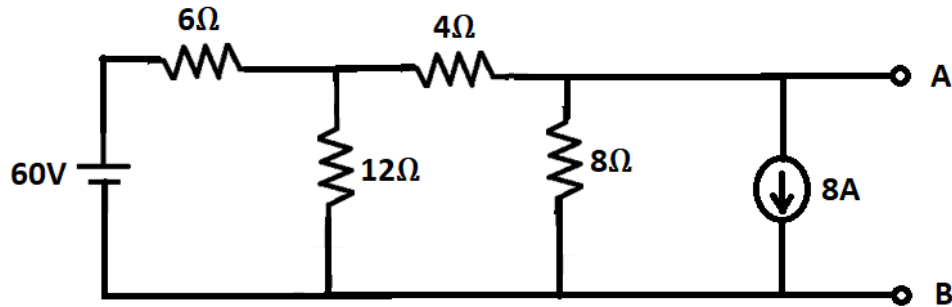
Obtain the Thevenin's Equivalent across the terminals A & B for the network given.



Solution:

Note: In this network, there is no load resistance. Entire network needs to be replaced with its Thevenin's Equivalent i.e., V_{TH} in series with R_{TH} .

Finding V_{TH} :

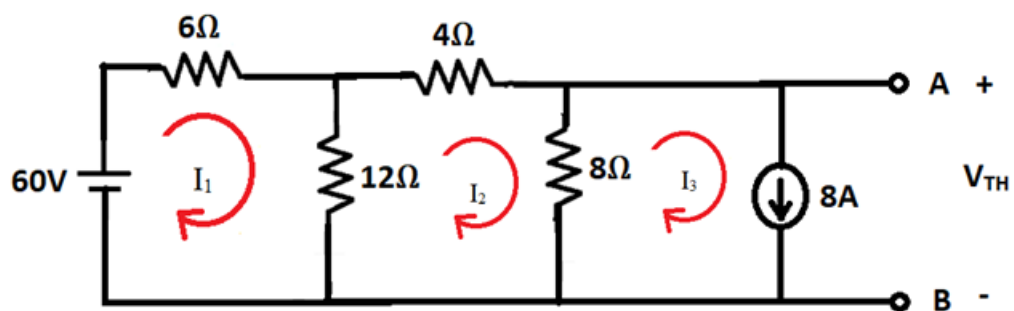

$$\text{KVL (Mesh 1)} : 18I_1 - 12I_2 - 0I_3 = 60 \quad \text{---- (1)}$$


$$\text{KVL (Mesh 2)} : -12I_1 + 24I_2 - 8I_3 = 0 \quad \text{---- (2)}$$

$$\text{Current Equation (Mesh 3)} : I_3 = 8 \quad \text{---- (3)}$$

Solving (1), (2) & (3), $I_1 = 7.66\text{A}$; $I_2 = 6.5\text{A}$

$$\text{Hence, } V_{TH} = (I_2 - I_3) * 8\Omega = -12\text{V}$$


Finding R_{TH} :

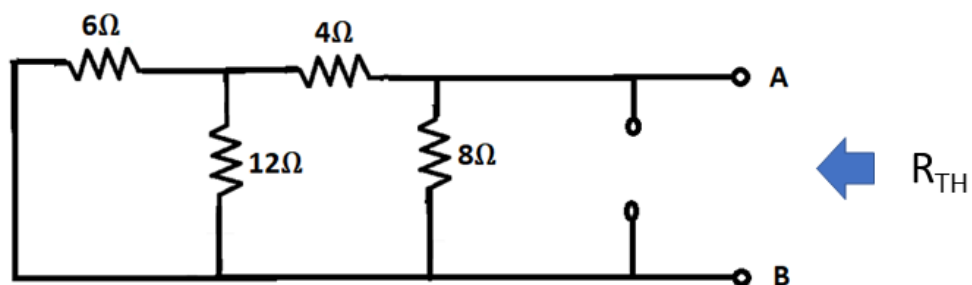

Unit I: DC Circuits

Hence, $R_{TH} = \{(6\Omega \parallel 12\Omega) + 4\Omega\} \parallel 8\Omega = 4\Omega$

Thevenin's Equivalent Circuit:

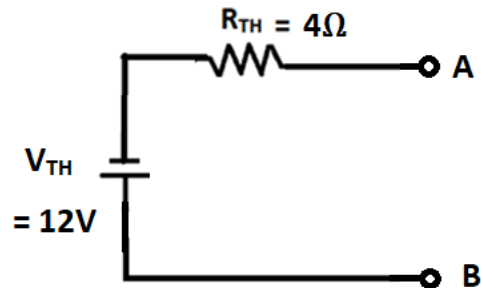

Here, since V_{TH} has turned out to be negative, it can be represented in the equivalent network with battery polarity reversed.