


## Unit I: DC Circuits

### Notes Class- 14

#### Thevenin's Theorem:
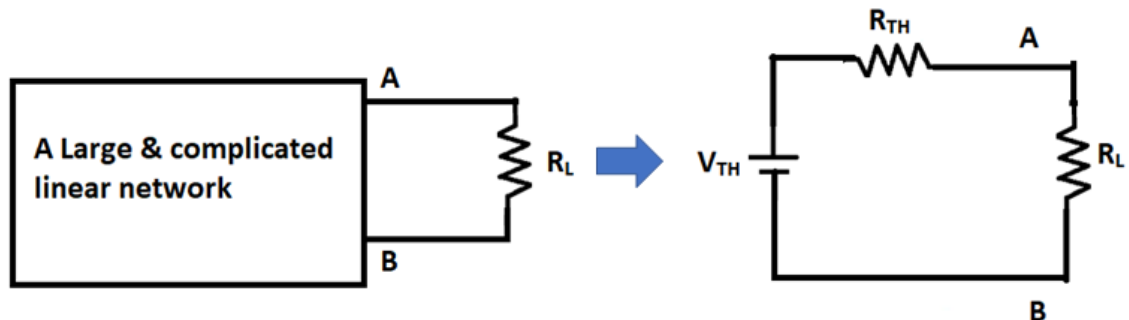
##### Statement:

"A linear network with a large number of independent and dependent sources and resistors between two terminals can be replaced with a simple two element series equivalent in which a voltage source called 'Thevenin's Equivalent Voltage' ( $V_{TH}$ ) is in series with a resistance called 'Thevenin's Equivalent Resistance' ( $R_{TH}$ )."



#### Steps to find Thevenin's Voltage & Thevenin's Resistance

##### Steps to find $V_{TH}$ :

Step 1: Remove the load resistance.

Step 2: Mark voltage across open load terminals and designate it as  $V_{TH}$ .

Step 3: Find  $V_{TH}$  using KVL or any other technique.

##### Steps to find $R_{TH}$ :

Step 1: Remove the load resistance.

Step 2: Replace all independent voltage sources with short circuit & all independent current sources with open circuit


Step 3: Looking into the open load terminals find the equivalent resistance.

**Note:** Load resistance is that resistance in which we need to find current or voltage or power response.

#### Numerical Example 1:


Using Thevenin's Theorem, calculate the range of current flowing through the resistance  $R$ , as it varies from  $6\Omega$  and  $36\Omega$ .

## Unit I: DC Circuits

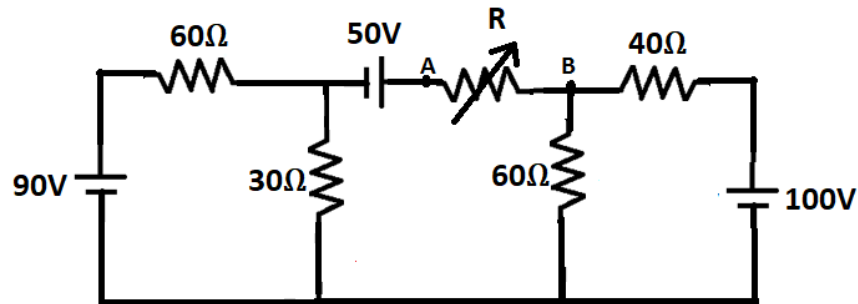

**Solution:**

**Finding  $V_{TH}$  :**

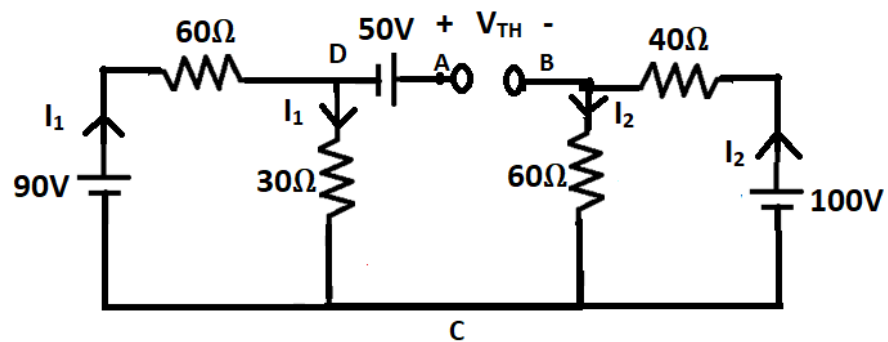


90V - 60Ω - 30Ω makes a simple series path. 100V - 40Ω - 60Ω makes another simple series path.

$$\text{Hence, } I_1 = \frac{90V}{90\Omega} = 1A ; I_2 = \frac{100V}{100\Omega} = 1A$$

$$\text{By KVL (DABCD), } +50 - V_{TH} - 60 \cdot I_2 + 30 \cdot I_1 = 0$$

$$V_{TH} = 20V$$

**Finding  $R_{TH}$  :**

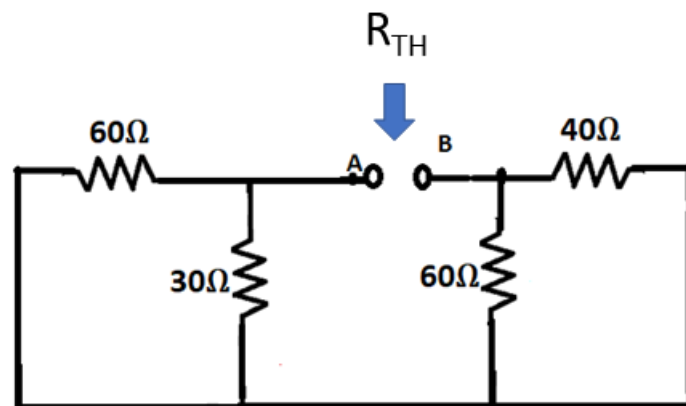


## Unit I: DC Circuits

Here, ( $60\Omega$  and  $30\Omega$ ) are in parallel. Also, ( $60\Omega$  and  $40\Omega$ ) are in parallel. These two parallel combinations are in series.

Hence,  $R_{TH} = (60\Omega \parallel 30\Omega) + (60\Omega \parallel 30\Omega) = 44\Omega$

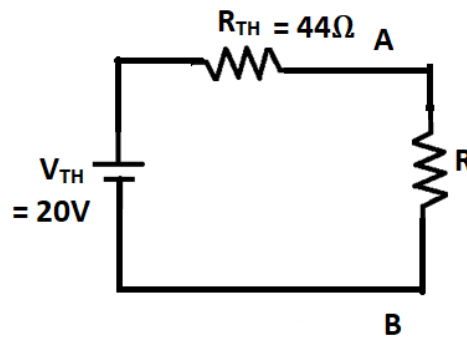Let us now replace the original network with its Thevenin's Equivalent i.e.,



Hence, Load current  $I_L = \frac{V_{TH}}{R_{TH} + R}$

When  $R = 6\Omega$ ,  $I_L = 0.4A$

When  $R = 36\Omega$ ,  $I_L = 0.25A$

Hence, current through 'R' ranges from 0.25A to 0.4A.