

ELEMENTS OF ELECTRICAL ENGINEERING

Course Code : UE25EE141A/B



FACULTY CONTRIBUTED:

Department of EEE, RR Campus

Prof . Jyothi T N

Prof. Vadhiraj K P P

Prof. Kruthika N

Prof. Suma S

Prof. Pushpa K R

Prof. Sangeeta Modi

Department of ECE, EC Campus

Prof. Lokesh L

Prof. Dhanashree G Bhate

Dr. Renuka R Kajur

Prof. Rajesh Chandrashekar

Prof. Sangam Kumar G H

Balanced Star Connected Three Phase System – Numerical Examples

Jyothi T.N

Department of Electrical & Electronics Engineering

Numerical Example 1

Question:

A balanced 3 Φ , star connected load of 100KW takes a leading current of 80A when connected to a 3 Φ , 1.1KV, 50Hz supply. Find the resistance, impedance and the capacitance of the load per phase. Also calculate the power factor of the load.

Solution :

Given Data:

Line voltage, $V_L = 1.1\text{KV}$; $f = 50\text{Hz}$

Line current, $I_L = 80\text{A}$

Three phase Active Power, $P_{3\text{-phase}} = 100\text{KW}$

Numerical Example 1 (contd..)

Calculations:

Since star connected system,

Phase current, $I_{ph} = I_L = 80A$

And Phase voltage, $V_{ph} = \frac{V_L}{\sqrt{3}} = 635.08V$

Impedance per phase, $Z = \frac{V_{ph}}{I_{ph}} = 7.94\Omega$

$P_{3-phase} = 100KW = 3 * I_{ph}^2 * R$; Hence, $R = 5.21\Omega$

Capacitive reactance per phase, $X_C = \sqrt{(Z^2 - R^2)} = 5.99\Omega$

Hence, Capacitance per phase, $C = \frac{1}{\omega X_C} = 531.25\mu F$

Powerfactor of the load, $\cos\phi = \frac{R}{Z} = 0.656$ Lead

Numerical Example 1 (contd..)

Alternative solution:

Since star connected system, Phase current, $I_{ph} = I_L = 80A$

And Phase voltage, $V_{ph} = \frac{V_L}{\sqrt{3}} = 635.08V$

Impedance per phase, $Z = \frac{V_{ph}}{I_{ph}} = 7.94\Omega$

$$P_{3-phase} = 100KW = \sqrt{3} * V_L * I_L * \cos(\phi)$$

Hence, Powerfactor of the load, $\cos\phi = 0.656$ Lead

Resistance per phase, $R = Z * \cos\phi = 5.21\Omega$

Capacitive reactance per phase, $X_C = \sqrt{(Z^2 - R^2)} = 5.99\Omega$

Hence, Capacitance per phase, $C = \frac{1}{\omega X_C} = 531.25\mu F$

1. A balanced 3 ϕ star connected load is supplied from a symmetrical 3 ϕ 400V system. The current in each phase is 30A and lags by 30° behind the voltage. Find i) Impedance in each phase ii) total power drawn. Draw phasor diagram.

Text Book:

1. **“Basic Electrical Engineering” S.K Bhattacharya, 1stEdition Pearson India Education Services Pvt. Ltd., 2017**
2. **“Basic Electrical Engineering”, D. C. Kulshreshta, 2ndEdition, McGraw-Hill. 2019**
3. **“Special Electrical Machines” E G Janardanan, PHI Learning Pvt. Ltd., 2014**

Reference Books:

1. **“Engineering Circuit Analysis” William Hayt, Jack Kemmerly, Jamie Phillips and Steven Durbin, 10th Edition McGraw Hill, 2023**
2. **“Electrical and Electronic Technology” E. Hughes (Revised by J. Hiley, K. Brown & I.M Smith), 12th Edition, Pearson Education, 2016.**



THANK YOU

Jyothi T N

Department of Electrical & Electronics Engineering

jyothitn@pes.edu