

Unit I: Assessment: Assignments

Assignment – Lecture 7

1. Prove that equal delta connected resistors when transformed to equivalent star become one-third each.
2. Prove that equal star connected resistors when transformed to equivalent delta become thrice each.