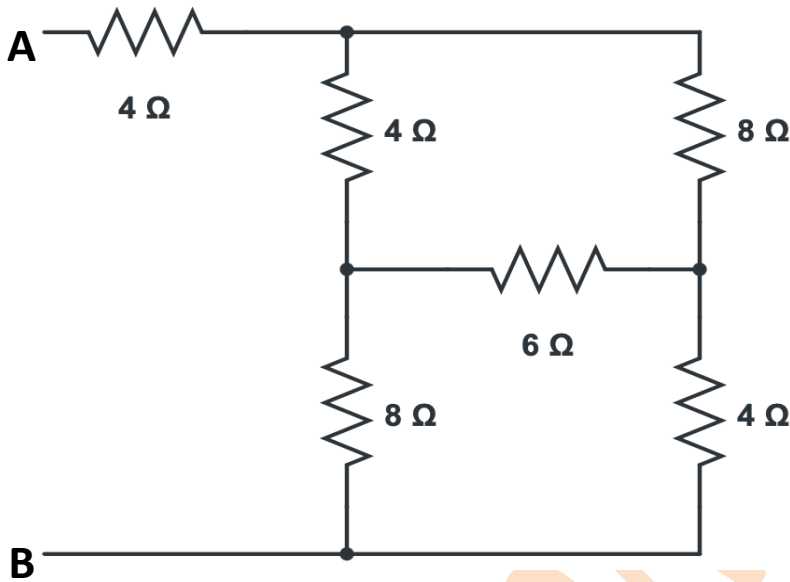




Unit I: Assessment: Q & A (Selected)

Lecture 8

- Find the equivalent resistance between the terminals A and B in the given network.



SOLUTION:

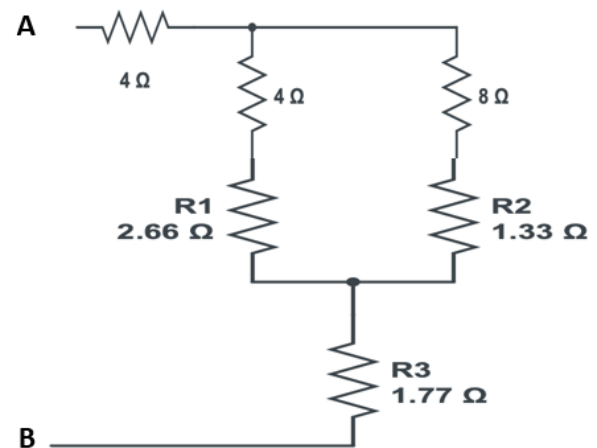
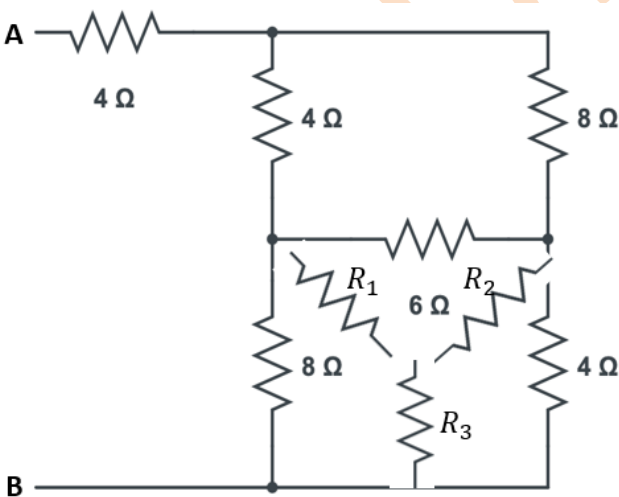


$$R_1 = \frac{8 \times 6}{8 + 6 + 4} = 2.66 \Omega$$

$$R_2 = \frac{6 \times 4}{8 + 6 + 4} = 1.33 \Omega$$

$$R_3 = \frac{8 \times 4}{8 + 6 + 4} = 1.77 \Omega$$

Unit I: Assessment: Q & A (Selected)

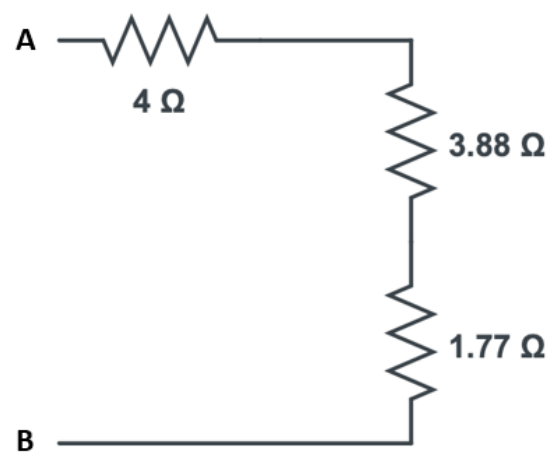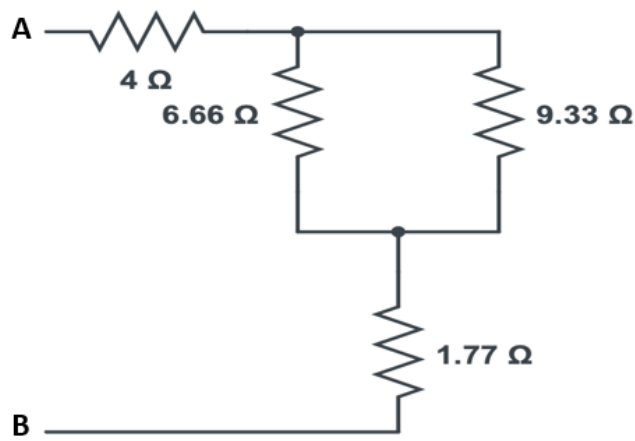

$$\frac{6.66 \times 9.33}{6.66 + 9.33} = 3.88\Omega$$

$$R_{AB} = 4 + 3.88 + 1.77 = 9.65\Omega$$