

Unit I: Assessment: Assignments

Assignment – Lecture 9

1. Find the equivalent resistance between the terminals A & B in the given network:

