


Unit I: DC Circuits

NOTES – CLASS 8


Numerical Examples on Star Delta Transformations:

Numerical Example 1:

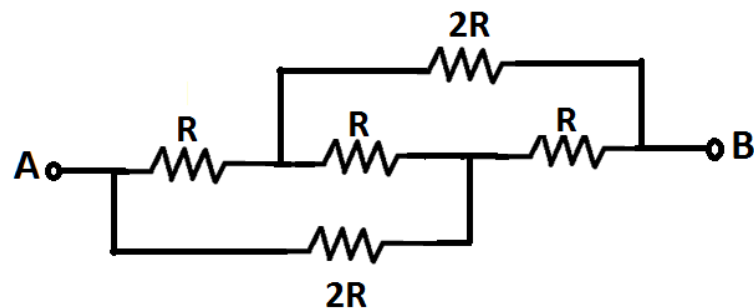
Find the equivalent resistance between the terminals A & B in the given network.



Solution:

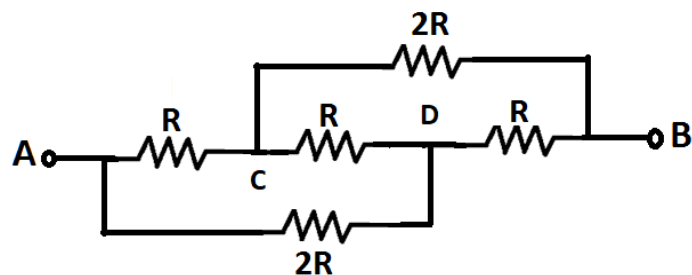

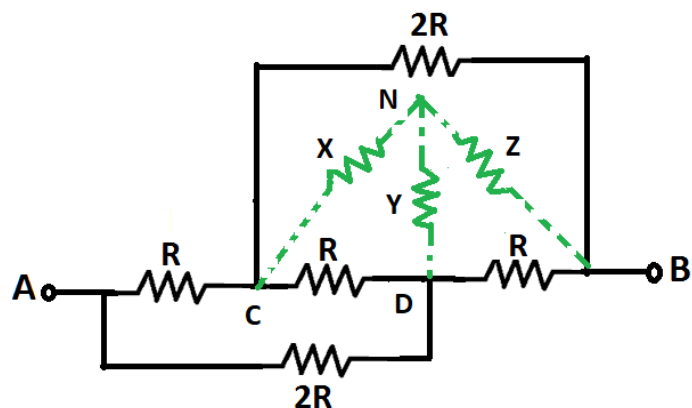Transform Delta existing between the terminals C-D-B into its equivalent star



The equivalent star resistors can be obtained as


Unit I: DC Circuits

$$X = \frac{R \cdot 2R}{(R + 2R + R)} = \frac{R}{2} \Omega$$


$$Y = \frac{R \cdot R}{(R + 2R + R)} = \frac{R}{4} \Omega$$

$$Z = \frac{R \cdot 2R}{(R + 2R + R)} = \frac{R}{2} \Omega$$


Hence, the network reduces as follows:

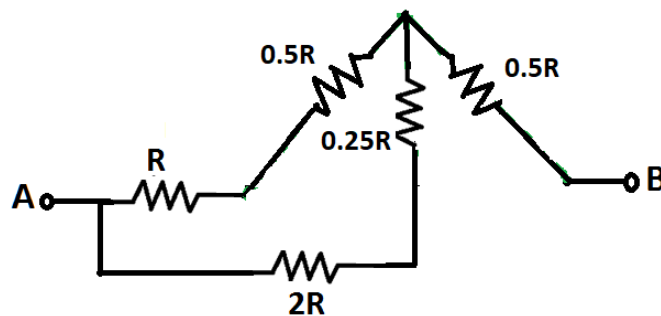

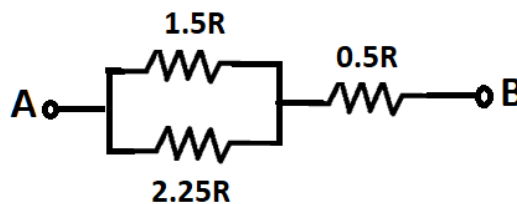Now, combine (R & $0.5R$) in series and ($2R$ & $0.25R$) in series. It gives



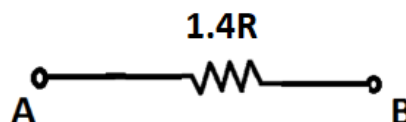Now, combine ($1.5R$ & $2.25R$) in parallel & then, combine its equivalent in series with $0.5R$.




Hence, the equivalent resistance is $1.4R$


Numerical Example 2:

Find the equivalent resistance between the terminals A & B in the network shown.


Unit I: DC Circuits

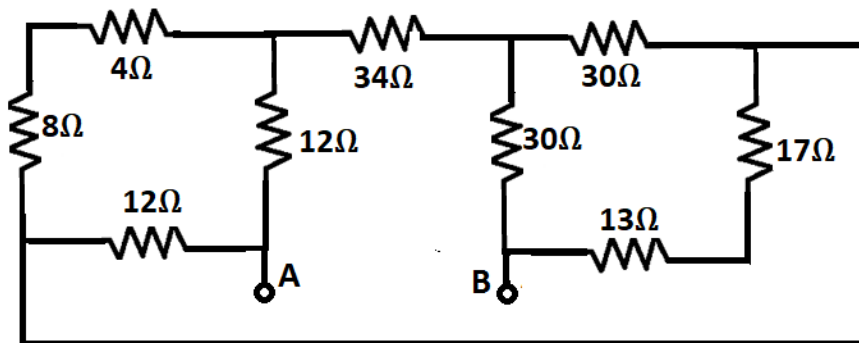

Solution:

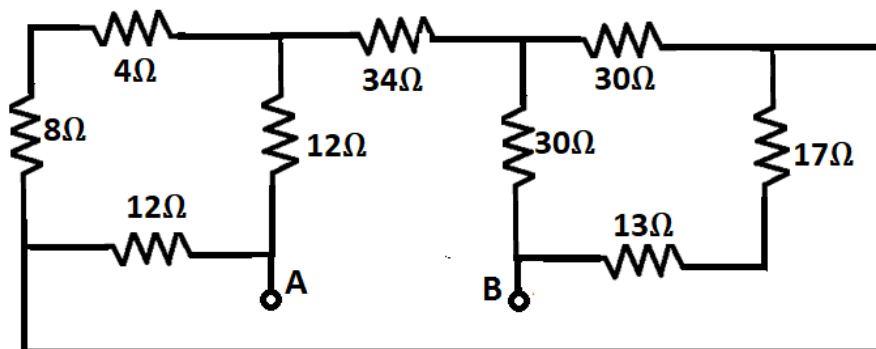


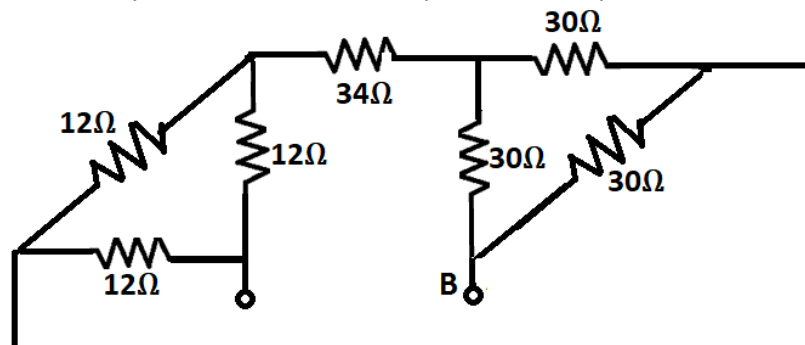Combining (8Ω & 4Ω) in series and also (13Ω & 17Ω) in series,




Now, transform $12\Omega - 12\Omega - 12\Omega$ delta into its equivalent star and also $30\Omega - 30\Omega - 30\Omega$ delta into its equivalent star,

Unit I: DC Circuits

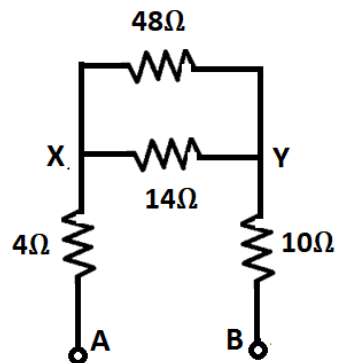


Now, combine 48Ω and 14Ω in parallel

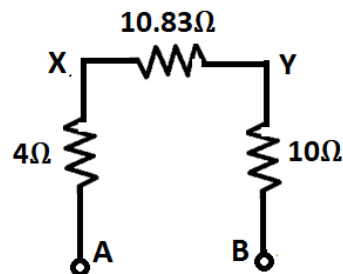

Now, combine all of them in series, which gives $R_{AB} = 24.83\Omega$


Numerical Example 5:

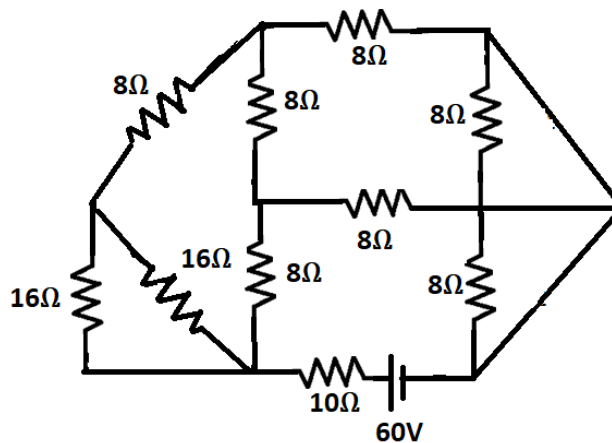Find the voltage drop across 10Ω resistor in the network shown.




Solution:


Unit I: DC Circuits

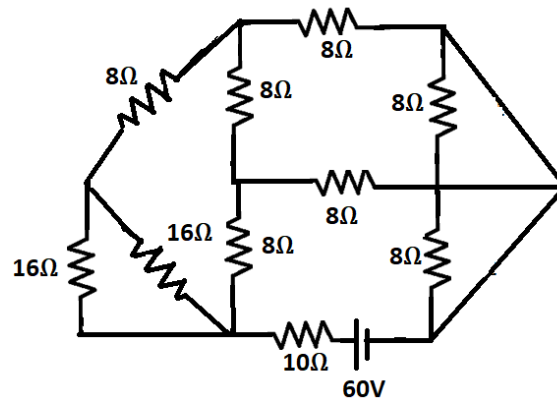

Combine 16Ω & 16Ω in parallel

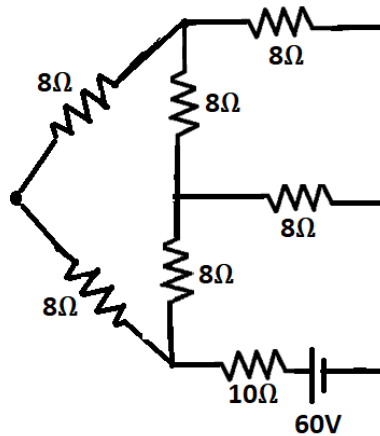


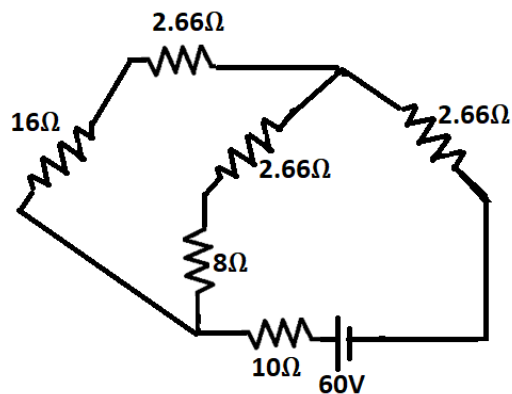Combine left extreme 8Ω & 8Ω in series. Also, transform top delta (8Ω - 8Ω - 8Ω) into equivalent star




Now, 16Ω and 2.66Ω are in series. Also, 8Ω and 2.66Ω are in series.

Unit I: DC Circuits

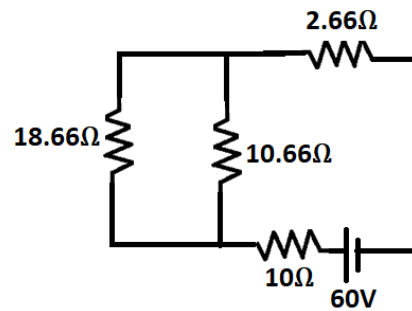

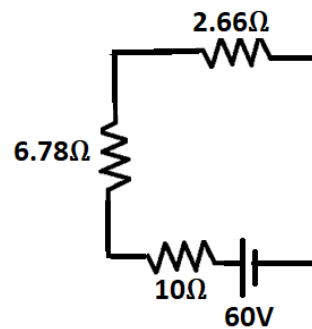Now combine 18.66Ω and 10.66Ω in parallel.



Now, remaining resistors are in series, which gives $R_{eq} = 19.44\Omega$

Current delivered by 60V source, $I_S = \frac{60}{R_{eq}} = \frac{60}{19.44} = 3.086A$

Voltage drop across 10Ω resistor = $I_S * 10 = 30.86V$