

# ELEMENTS OF ELECTRICAL ENGINEERING

## Course Code : UE25EE141A/B



### FACULTY CONTRIBUTED:

Department of EEE, RR Campus

Prof . Jyothi T N  
Prof. Vadhiraj K P P  
Prof. Kruthika N  
Prof. Suma S  
Prof. Pushpa K R  
Prof. Sangeeta Modi

Department of ECE, EC Campus

Prof. Lokesh L  
Prof. Dhanashree G Bhate  
Dr. Renuka R Kajur  
Prof. Rajesh Chandrashekar  
Prof. Sangam Kumar G H

# ELEMENTS OF ELECTRICAL ENGINEERING

---




## Balanced Delta Connected Three Phase System; Voltage and Current Relations

**Jyothi T.N**

Department of Electrical & Electronics Engineering

# ELEMENTS OF ELECTRICAL ENGINEERING

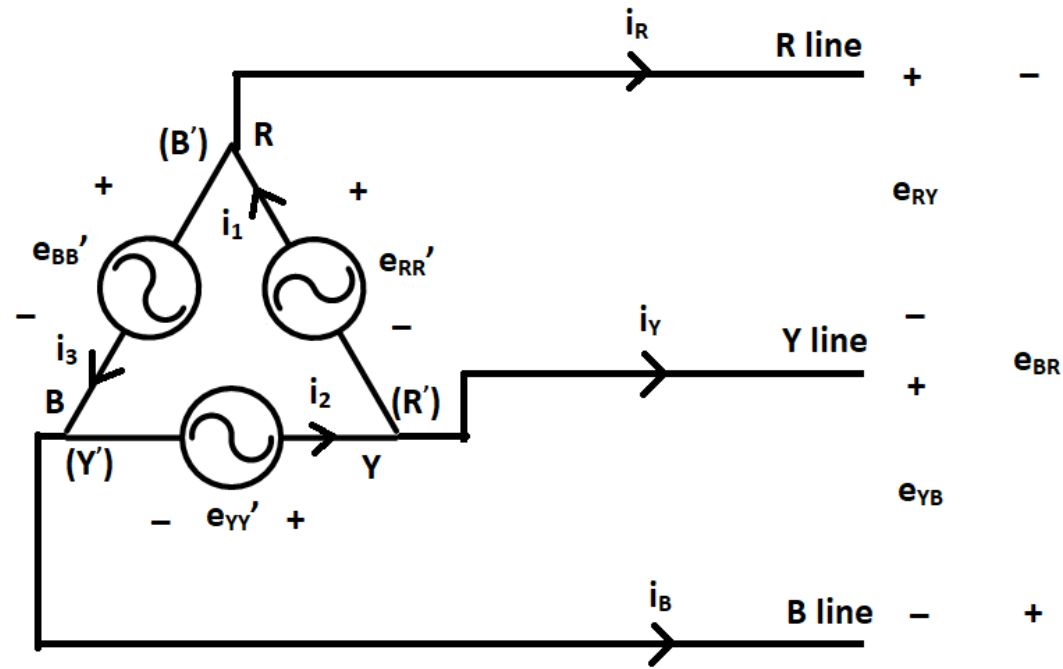
## Balanced Delta (or) Mesh Connected Three Phase System



- Coil R, Coil Y and Coil B are connected end to end to form a delta connected three phase system.
- $e_{RR'}$  ,  $e_{YY'}$  &  $e_{BB'}$  represent phase voltages.

# ELEMENTS OF ELECTRICAL ENGINEERING
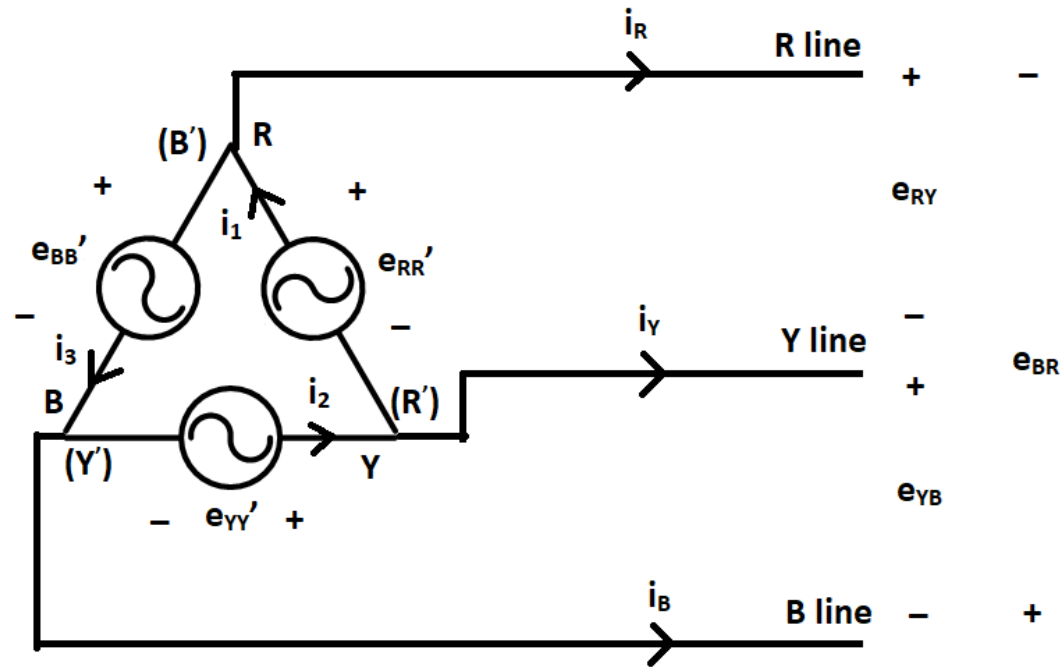
## Balanced Delta (or) Mesh Connected Three Phase System




- $e_{RY}$ ,  $e_{YB}$  &  $e_{BR}$  represent Line (or) Line to line voltages.
- $i_1$ ,  $i_2$  &  $i_3$  represent phase currents.
- $i_R$ ,  $i_Y$  &  $i_B$  represent line currents.

# ELEMENTS OF ELECTRICAL ENGINEERING
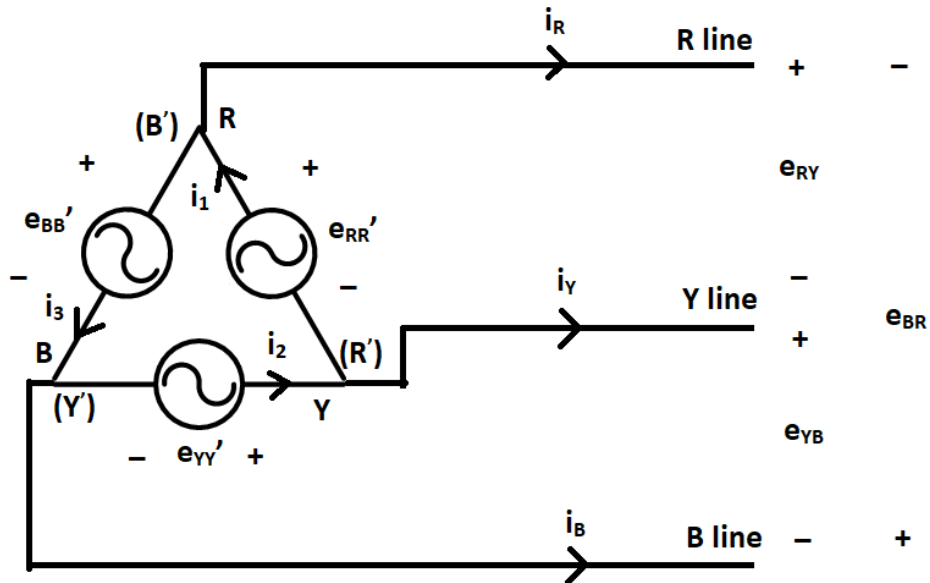
## Relation between Line & Phase voltages – Balanced Delta System



In a balanced delta connected three phase system,



Line voltage = Phase voltage


$$\text{i.e., } e_{RY} = e_{RR'}$$

$$e_{YB} = e_{YY'}$$

$$e_{BR} = e_{BB'}$$

# ELEMENTS OF ELECTRICAL ENGINEERING
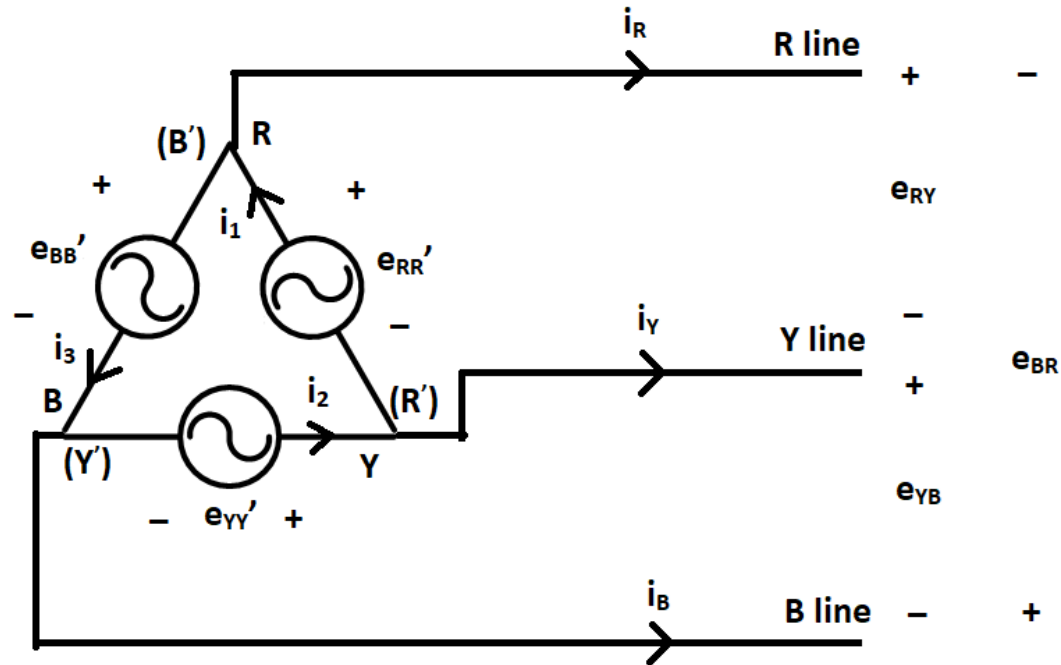
## Relation between Line & Phase currents – Balanced Delta System



By KCL at R,  $i_1 = i_R + i_3$

Hence,  $i_R = i_1 - i_3$

$$\overline{I_R} = \overline{I_1} - \overline{I_3}$$

$$\overline{I_1} = \frac{I_m}{\sqrt{2}} \angle 0^\circ = I_{ph} \angle 0^\circ$$

where,  $I_{ph}$  is the RMS value of phase current.

$$\overline{I_2} = \frac{I_m}{\sqrt{2}} \angle -120^\circ = I_{ph} \angle -120^\circ$$

$$\overline{I_3} = \frac{I_m}{\sqrt{2}} \angle -240^\circ = I_{ph} \angle -240^\circ$$

$$\overline{I_R} = I_{ph} \angle 0^\circ - I_{ph} \angle -240^\circ$$

$$= I_{ph} (1 - (\cos 240^\circ - j \sin 240^\circ))$$

$$= I_{ph} \left( \frac{3}{2} - j \frac{\sqrt{3}}{2} \right)$$

$$= \sqrt{3}I_{ph}(\cos 30^\circ - j\sin 30^\circ)$$

$$= \sqrt{3}I_{ph} \angle -30^\circ$$

$$\overline{I_Y} = \overline{I_2} - \overline{I_1} = \sqrt{3}I_{ph} \angle -150^\circ$$

$$\overline{I_B} = \overline{I_3} - \overline{I_2} = \sqrt{3}I_{ph} \angle -270^\circ$$

Thus, in a balanced delta connected three phase system,


(i) Magnitude (RMS value) of Line current =  $\sqrt{3}$  \* (Magnitude of Phase current)


(ii) Each line current lags the corresponding phase current by  $30^\circ$



# ELEMENTS OF ELECTRICAL ENGINEERING
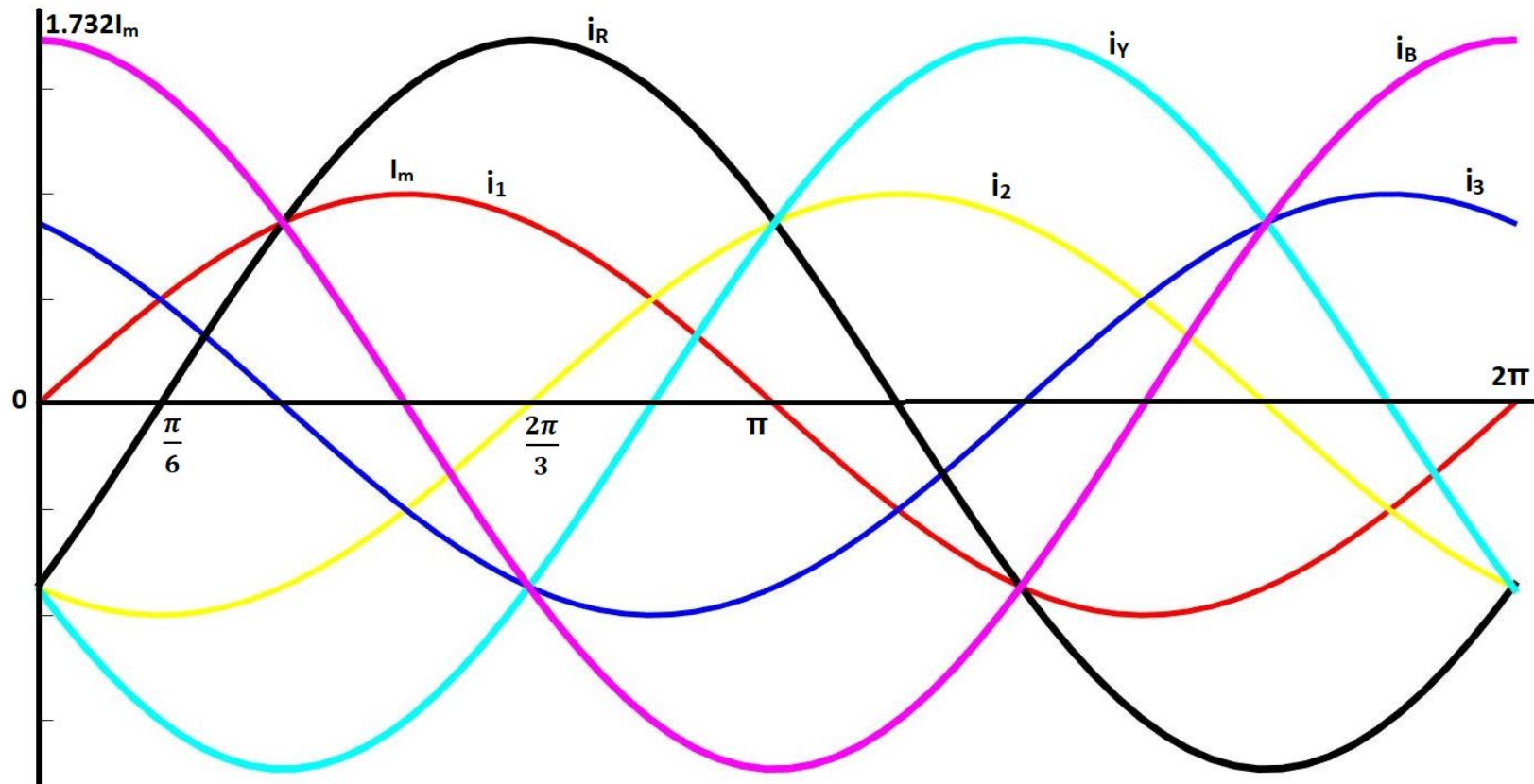
## Balanced Delta System – Line and Phase Current Waveforms



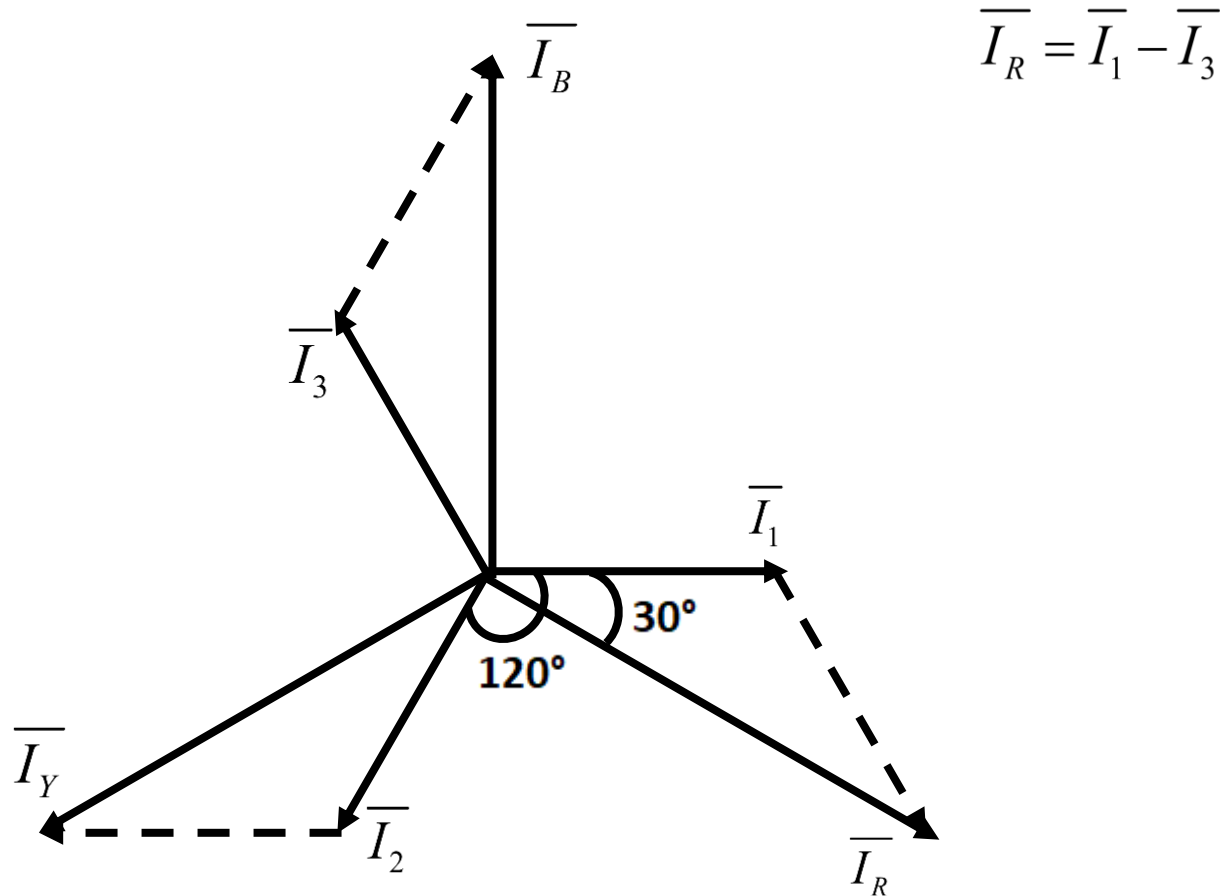

1) Three similar elements are connected in delta across 2000V, 50HZ three phase supply. Load has power factor of 0.5 . Current taken is 100A leading. Find the values of circuit parameters.

### **Text Book:**

1. **“Basic Electrical Engineering” S.K Bhattacharya, 1<sup>st</sup>Edition Pearson India Education Services Pvt. Ltd., 2017**
2. **“Basic Electrical Engineering”, D. C. Kulshreshta, 2<sup>nd</sup>Edition, McGraw-Hill. 2019**
3. **“Special Electrical Machines” E G Janardanan, PHI Learning Pvt. Ltd., 2014**

### **Reference Books:**

1. **“Engineering Circuit Analysis” William Hayt, Jack Kemmerly, Jamie Phillips and Steven Durbin, 10<sup>th</sup> Edition McGraw Hill, 2023**
2. **“Electrical and Electronic Technology” E. Hughes (Revised by J. Hiley, K. Brown & I.M Smith), 12<sup>th</sup> Edition, Pearson Education, 2016.**



**THANK YOU**

---

**Jyothi T N**

Department of Electrical & Electronics Engineering

**[jyothitn@pes.edu](mailto:jyothitn@pes.edu)**