

Lecture 43

2. In a balanced delta connected three phase load, phase current is 10A and lags behind phase voltage 200V by 60° . Determine
- Three Phase Active Power
 - Three Phase Reactive Power
 - Three Phase Apparent Power

Solution

Given $I_{ph} = 20\text{ A}$
 $V_{ph} = 200\text{ V}$
 $\phi = 60^\circ$

Active power $P_{3\phi} = 3 V_{ph} I_{ph} \cos \phi$
 $= (3) (200) (20) \cos(60)$
 $= 6\text{ KW}$

Reactive power $Q_{3\phi} = 3 V_{ph} I_{ph} \sin \phi$
 $= 3 (200) (20) \sin(60)$
 $= 10.39\text{ KVAR}$

Apparent power $S_{3\phi} = 3 V_{ph} I_{ph}$
 $= 3 (200) (20)$
 $= 12\text{ KVA}$