

UE25EC141A - Electronic Principles and Devices (4-0-0-4-4)**Unit3: Question Bank**

- 1) Name the different terminals of transistor and explain them briefly.(4 Marks)
- 2) Write a brief note on the following (6 Marks)
 - (i) Active region
 - (ii) Saturation region
 - (iii) Cut-off region
 - (iv) Inversely active region
- 3) What is Base width modulation with respect to common base configuration.(4 Marks)
- 4) With a neat diagram explain Common base input- output characteristics (6 Marks)
- 5) With a neat diagram explain Common emitter input-output characteristics. (6 Marks)
- 6) Obtain the relationship between α and β (4 Marks)
- 7) Why biasing is required? (4 Marks)
- 8) Explain briefly operating point. (6 Marks)
- 9) Write a note on effects of temperature on Q-point (4 Marks)
- 10) With mathematical interpretations explain Fixed bias configuration (6 Marks)
- 11) With mathematical interpretations explain Emitter bias configuration (6 Marks)
- 12) Explain with mathematical interpretations Voltage divider bias configuration (7 Marks)
- 13) Explain Single Stage CE Amplifier. (6 Marks)
- 14) With a neat diagram explain the Common Mode operation in Operational Amplifier [Op-Amp] (4 Marks)
- 15) Define the following with respect to Op-Amps (8 Marks)
 - (i) Input offset Voltage
 - (ii) Output offset Voltage
 - (iii) Input resistance
 - (iv) Output resistance
- 16) With a neat diagram explain Gain Bandwidth (4 Marks)
- 17) Determine the cut-off frequency of an-amp having specified values (2 Marks)
 $B1=1\text{MHz}$, $A_{VD}= 200 \text{ V/mV}$
- 18) Define the following with respect to op-amp (4 Marks)
 - (i) Slew rate
 - (ii) Common mode rejection ratio
- 19) Why negative feedback is necessary in Op-Amps? (4 Marks)
- 20) Explain the Virtual Ground concept. (4 Marks)
- 21) With relevant mathematical interpretation explain an Op-Amp inverting amplifier.(4 Marks)
- 22) With relevant mathematical interpretation explain an Op-Amp Non-inverting amplifier. (4 Marks)
- 23) With relevant mathematical interpretation explain an Op-Amp summing amplifier. (4 Marks)
- 24) With relevant mathematical interpretation explain an Op-Amp subtractor. (4 Marks)
- 25) Explain unity follower or voltage follower using Op-Amp (4 Marks)
- 26) What is the significance of voltage follower? (2 Marks)
- 27) With a neat diagram explain Comparators using op-amp (4 Marks)



PES UNIVERSITY

Dept. of Electronics and Communication Engineering