

Unit I: Assessment: Assignments

Assignment – Lecture 30

1. A parallel RLC circuit has a 10Ω resistor, 10mH inductor and 2mF capacitor connected in parallel across 20V, 50 Hz Ac supply. Determine
 - i) Admittance in each branch
 - ii) Total Admittance
 - iii) Magnitude of supply current